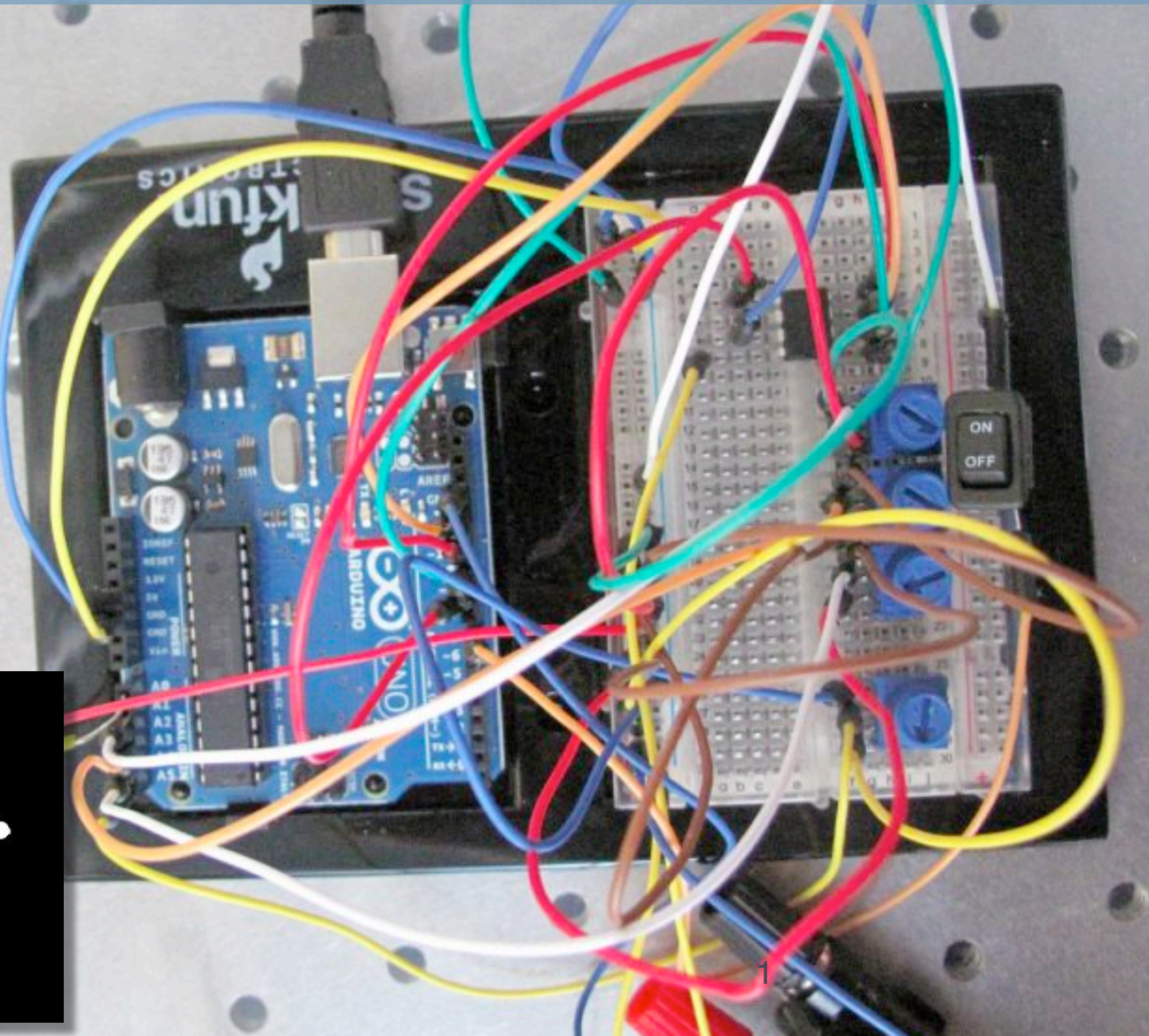


ES 50: Introduction to Electrical Eng.

Explore EE, satisfy a Gen Ed requirement & have fun



ES 50



... resistance is futile!

Lecture 5: Amplifiers (Part 2)

ES 50: Introduction to Electrical Engineering

Announcements

- ▶ **Review / problem sessions Wed & Thur
7-9:30PM moved to *MD119 lobby***

Last time...

- ▶ Dependent (voltage and current) sources
- ▶ Thevenin and Norton equivalent circuits
- ▶ Operational Amplifiers
 - ▶ Ideal characteristics
 - ▶ Realistic example
- ▶ Op-amp circuits

Today,


- ▶ More op-amp circuit topologies
- ▶ Several op-amp examples

Operational Amplifier “op-amp” summary


Important Characteristics:

- ▶ **One output terminal (V_o)**
 - ▶ Behaves as an ideal voltage source (i.e., no output resistance)
- ▶ **Two input terminals:**
 - ▶ positive (non-inverting):
if V_+ increases V_o **increases**
 - ▶ negative (inverting):
if V_- increases V_o **decreases**
 - ▶ $V_{in} = V_+ - V_-$
 - ▶ Input resistance between + and – terminal is extremely large!
- ▶ **Needs power supply**
 - ▶ Often not shown in ES 50 circuits


Op-amp showing power supply rails

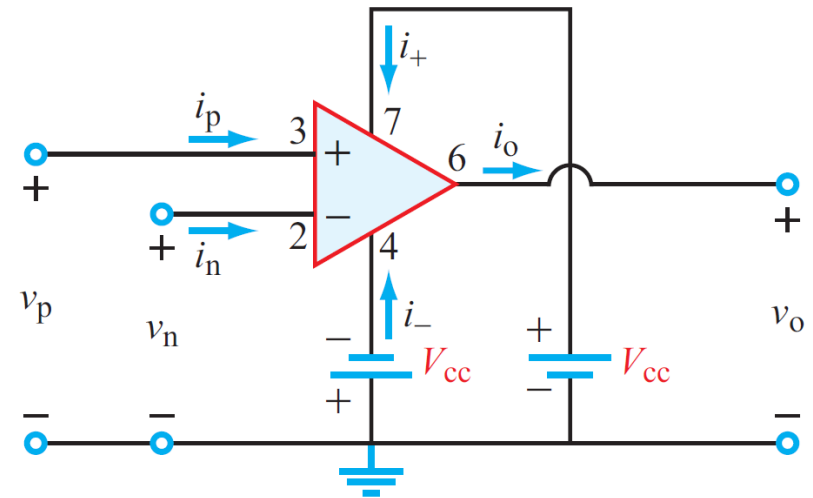

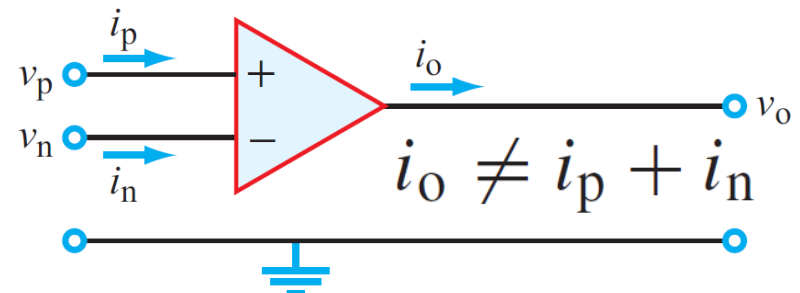Op Amp with power supply rails **not** shown
(how we usually show op-amps in ES 50)



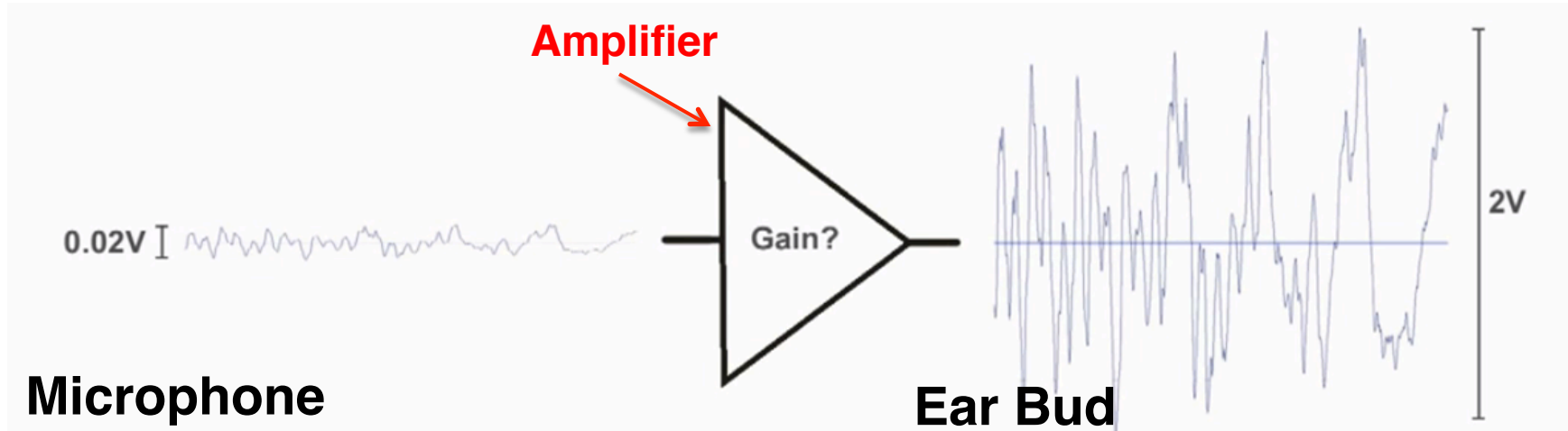
Example: Let's build an amplifier that picks up a heart beat and turns it into sound or flashing light



We need a gain of ~ 100 , but the op-amp has a gain of $A=10^6$.
What do we do?

Negative Feedback is used to control the gain

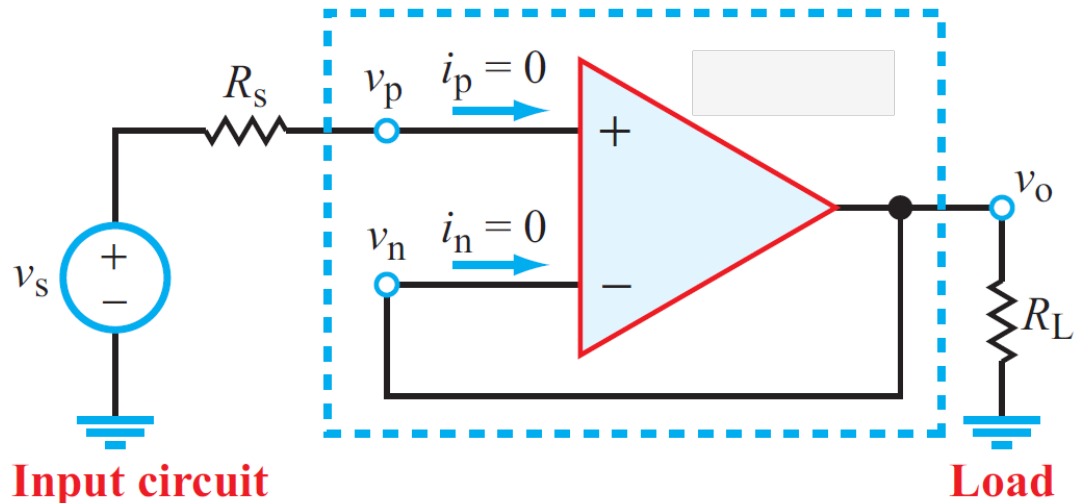- **Feedback:** Return some of the output to the input



- $v_n = v_o$ (shorted)

Op-Amp Golden rules:

- $i_p = 0 \rightarrow$ No voltage drop across $R_s \rightarrow v_p = v_s$

- $v_o = A * (v_p - v_n)$
then...

As $A \rightarrow \infty$ we get the following approximation:

$$v_o = A(v_s - v_o)$$

$$v_o(1 + A) = Av_s$$


$$v_o \approx v_s$$



$$v_o = v_s \frac{A}{1 + A}$$

Negative Feedback is used to control the gain

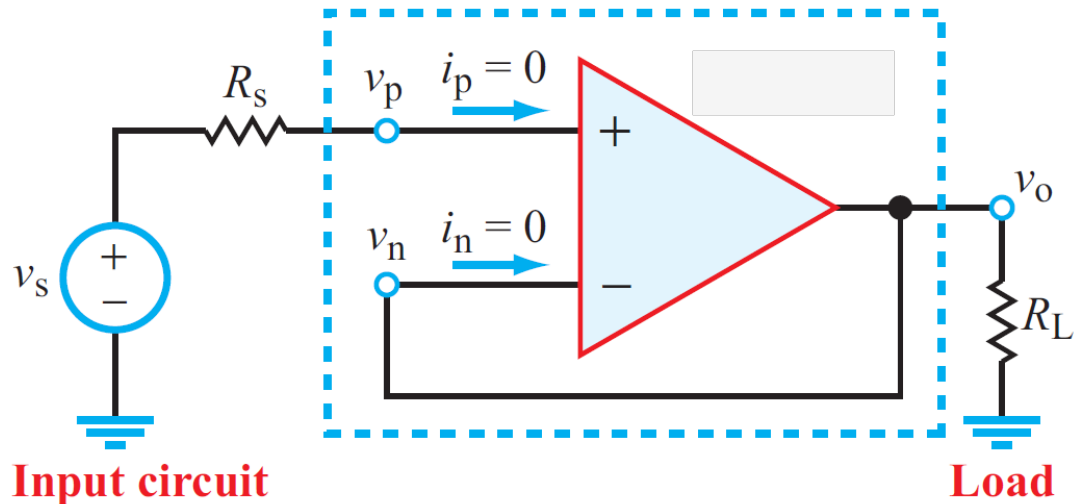- **Feedback:** Return some of the output to the input



As $A \rightarrow \infty$ we get the following approximation:


$$v_o = v_s$$

$$v_p = v_n$$

Also called a
unity-gain buffer or
voltage follower

Important property when
solving op-amp circuits

How can we get gain > 1 ?

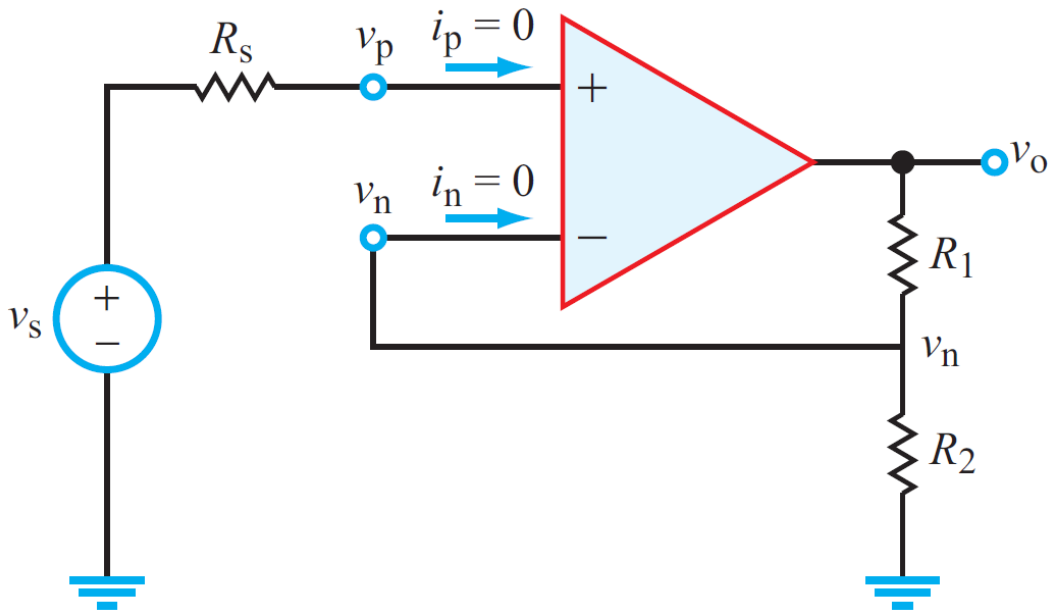

$$v_p = v_s$$

$$v_n = v_o \frac{R_2}{R_1 + R_2}$$

$$v_p = v_n$$

$$v_s = v_o \frac{R_2}{R_1 + R_2}$$


$$v_o = v_s \frac{R_1 + R_2}{R_2}$$

To get **closed-loop gain** $G = 100$:

- $R_1 = 99 * R_2$
- Let $R_1 = 100\text{k}\Omega \rightarrow R_2 = 1\text{k}\Omega$
(sensitive to accurate resistor values)

$$G = \frac{v_o}{v_s} = \frac{R_1 + R_2}{R_2}$$

Can find G using the node voltage method

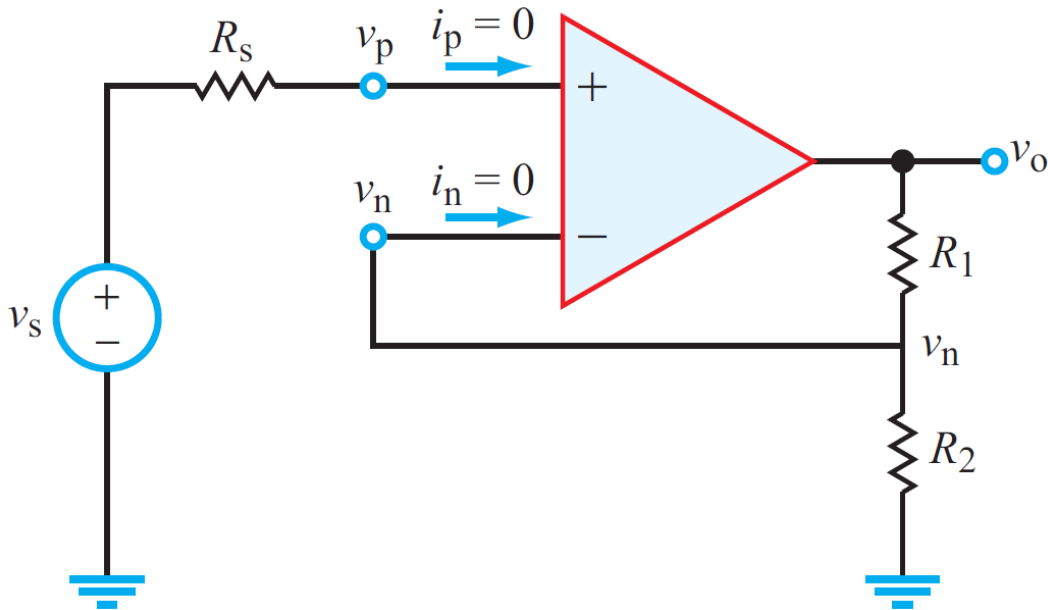

$$G = \frac{v_o}{v_s} = \frac{R_1 + R_2}{R_2}$$

Recall node voltage method:
Pick nodes w/ unknown voltage
and compute KCL

At node v_n :

$$\begin{aligned}\frac{v_o - v_n}{R_1} &= \frac{v_n}{R_2} + i_n \\ \frac{v_o}{R_1} &= v_n \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \\ v_o &= v_n \frac{R_1 + R_2}{R_2}\end{aligned}$$

At node v_p :


$$v_p = v_s$$

$$v_p = v_n$$

b/c $i_p = 0$


b/c $A = \infty$

Again, what's going on intuitively?

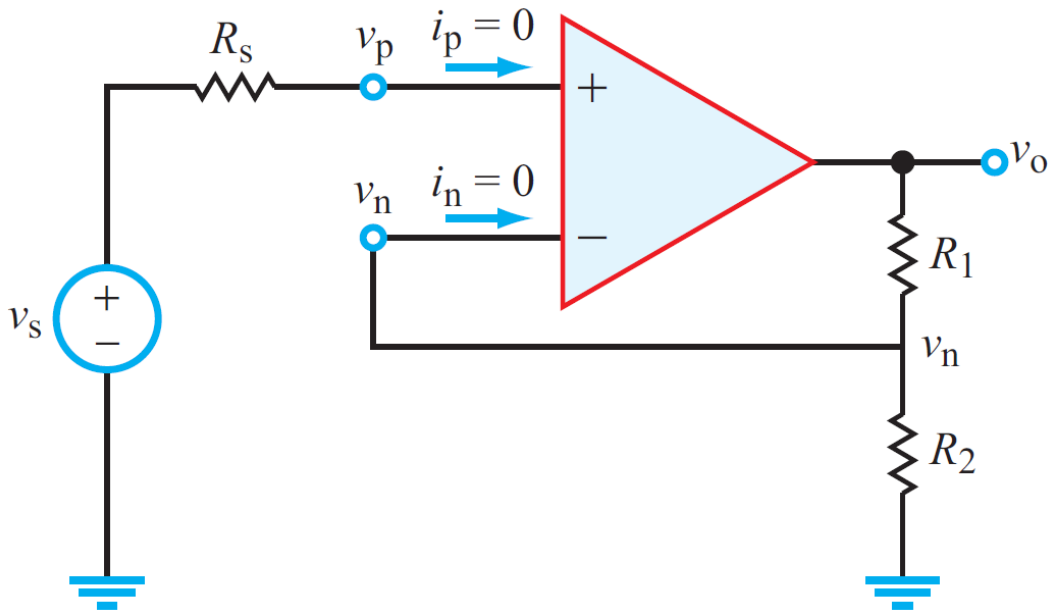

- ▶ Let's go around the loop one more time.
 - ▶ Assume v_s starts at 0V (v_o also at 0V) and increases by ΔV .
 - ▶ $v_p - v_n$ will increase by ΔV and cause the amplifier to drive v_o towards $A \cdot \Delta V$ and v_n towards $A \cdot \Delta V \cdot (R_2 / (R_1 + R_2))$.
 - ▶ But with negative feedback, we get $v_o / v_s = (R_1 + R_2) / R_2$.

And here is our heart-rate indicator 😊

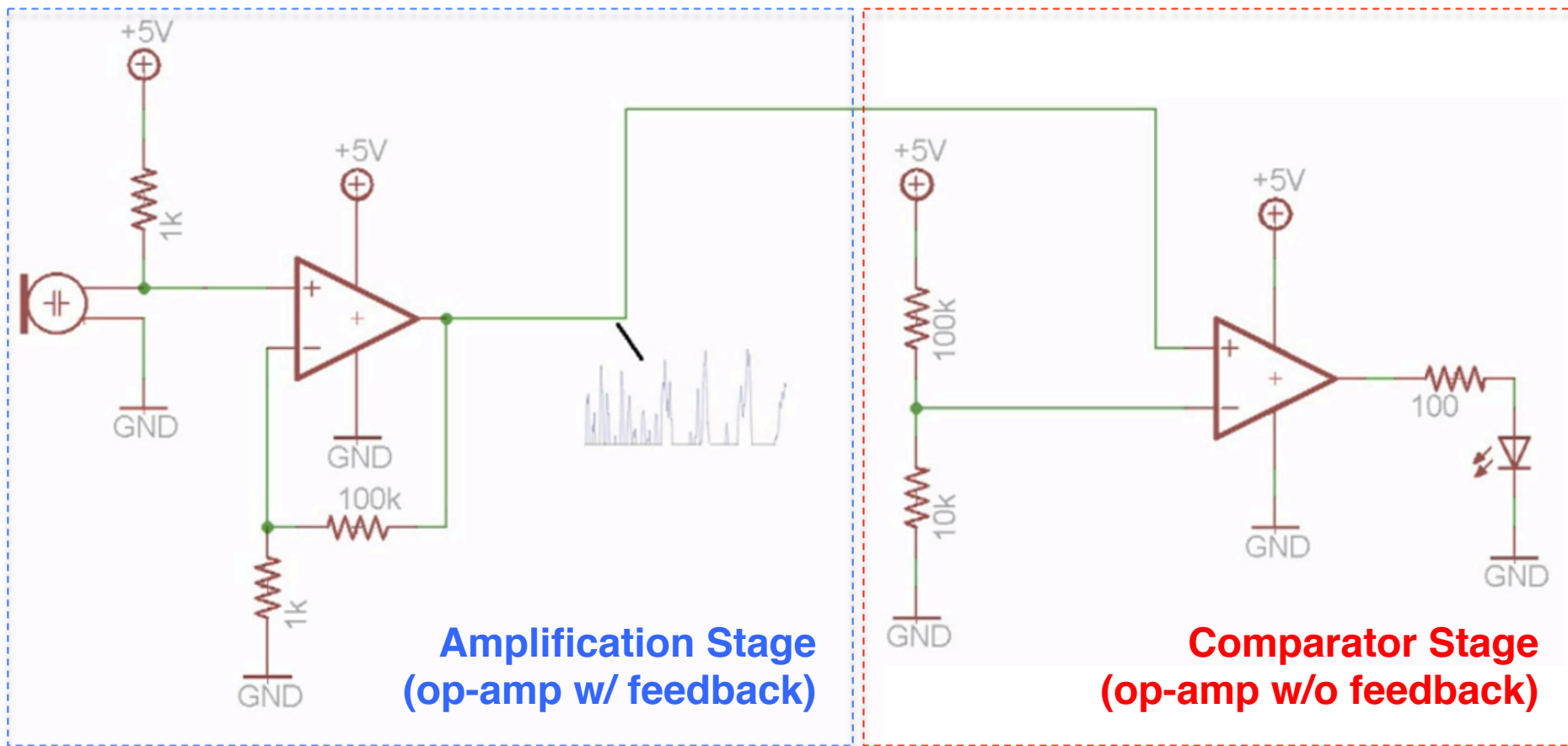


The same circuit can work as a clap-detector: <http://www.youtube.com/watch?v=y0Q0ERSP24A>
(also a very nice tutorial on op-amps!)

Music beat sensor: <http://www.youtube.com/watch?v=OTwg2Eal8x4>

Or, turn it into an Arduino-based heart rate monitor: <http://www.youtube.com/watch?v=5ekHuCT2a1M> 13

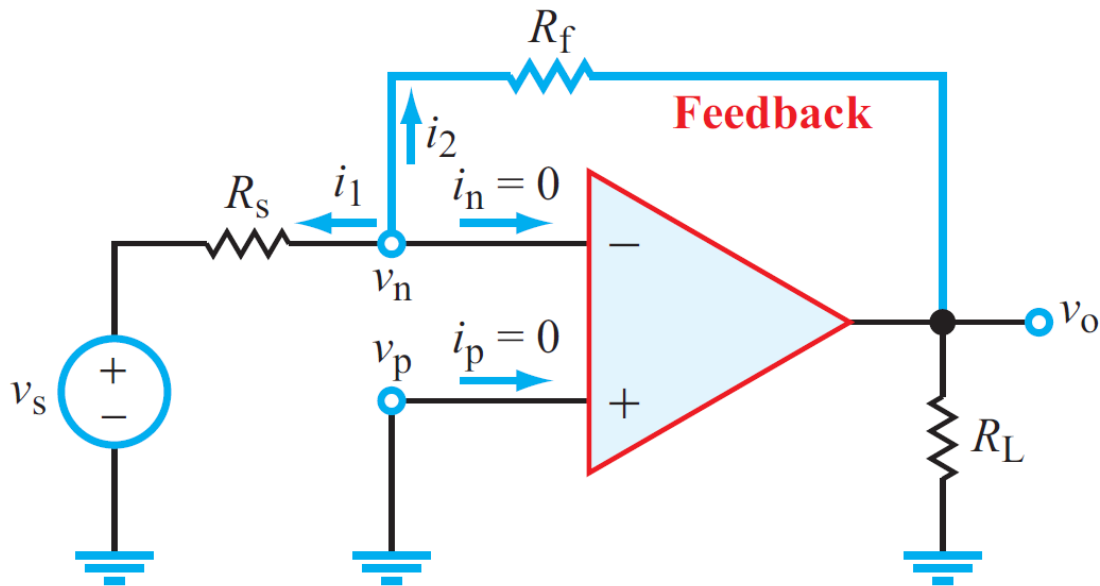Another very common topology: *Inverting Amplifier*



KCL at node v_n :

$$\frac{v_n - v_s}{R_s} + \frac{v_n - v_o}{R_f} + i_n = 0$$

$$v_n = v_p = 0$$


$$\frac{v_s}{R_s} + \frac{v_o}{R_f} = 0$$

Notice: Input, v_s , connected to the ***inverting*** input of the op-amp

$$G = \frac{v_o}{v_s} = -\frac{R_f}{R_s}$$

Inverting amplifier topology:
Negative closed-loop gain

Summing Amplifier

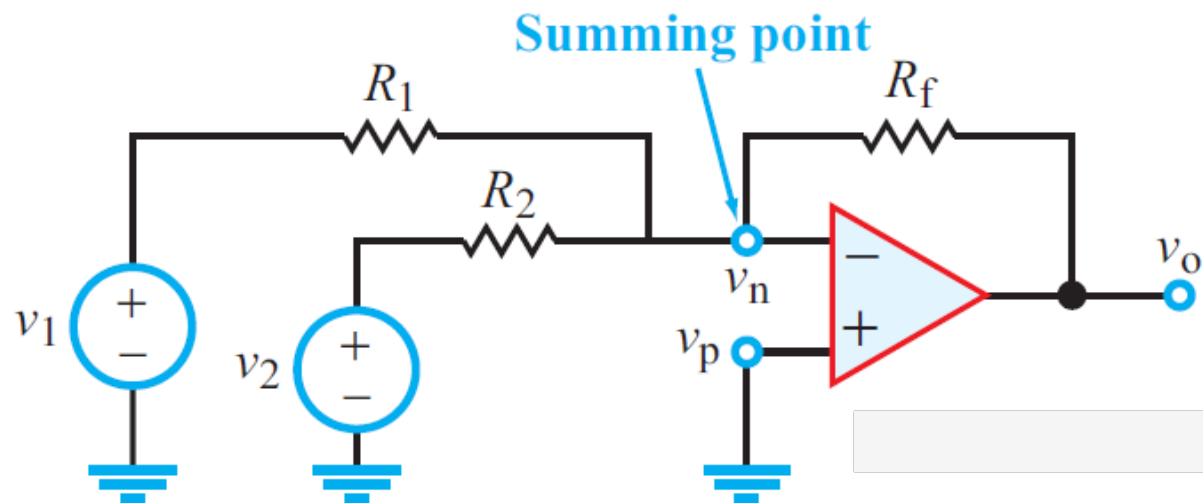


KCL at node v_n :

$$-\frac{v_o - v_n}{R_f} = \frac{v_1 - v_n}{R_1} + \frac{v_2 - v_n}{R_2}$$
$$-\frac{v_o}{R_f} = \frac{v_1}{R_1} + \frac{v_2}{R_2}$$

$$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2\right)$$


We could have also used superposition

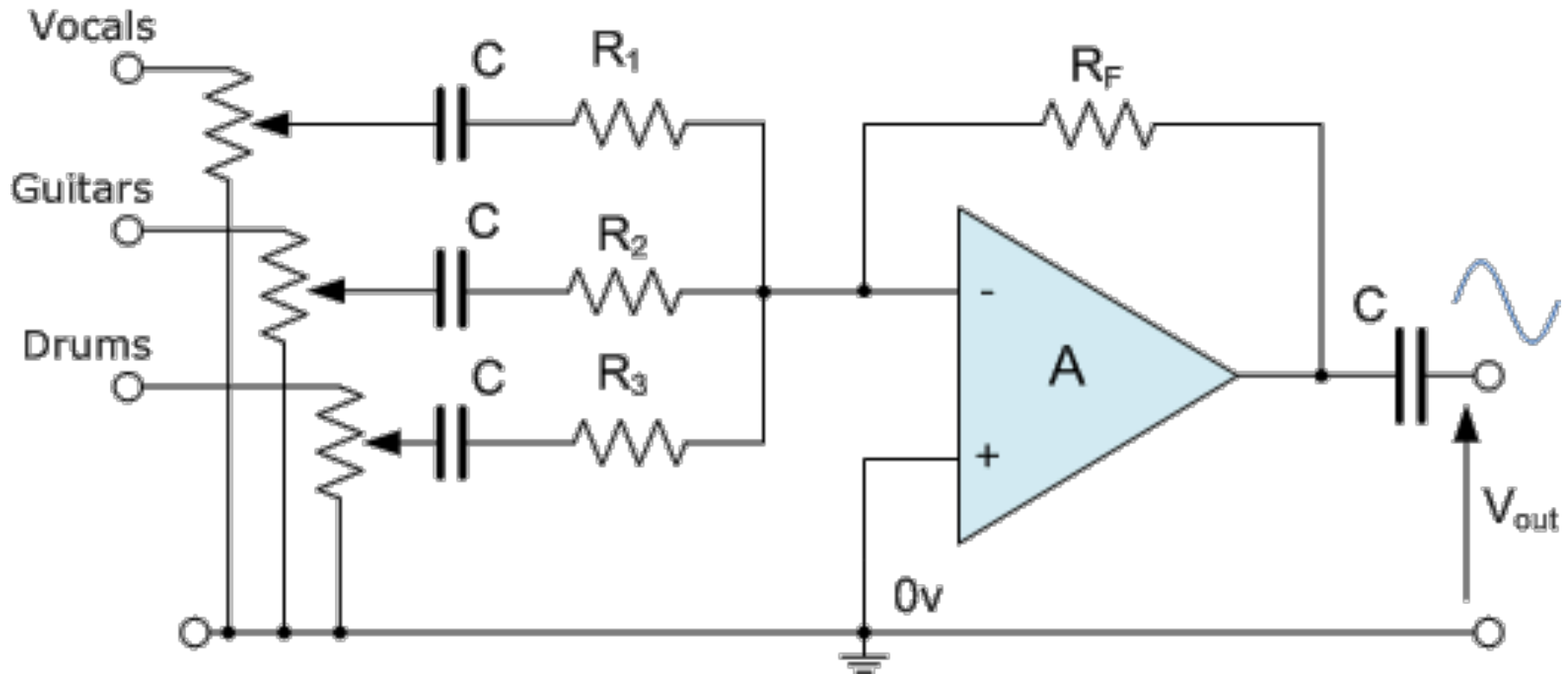Application of summing amplifier: **Music Mixer** (any DJs around?)













RC circuits are often used for filtering. Here, amplifier A amplifies a combination of the three incoming signals. Relative amplitudes set via potentiometers (voltage dividers).

Difference Amplifier – Details in HW

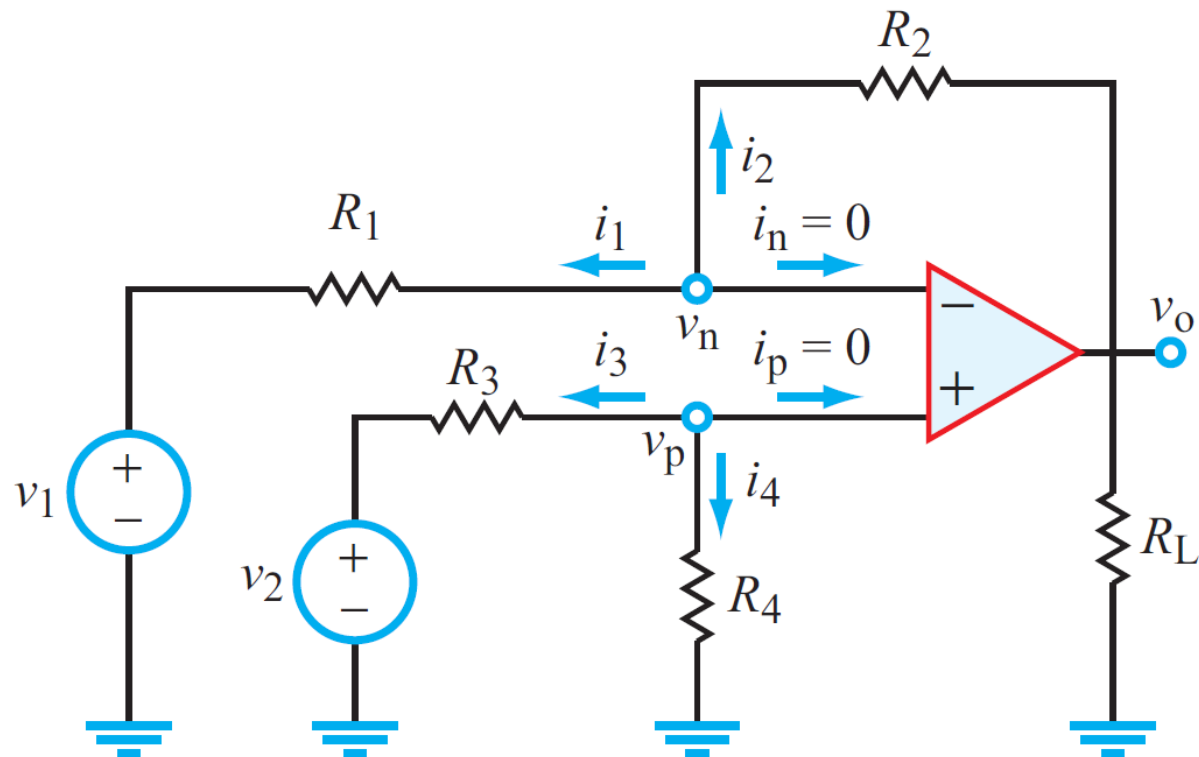


$$v_o = \left[\left(\frac{R_4}{R_3 + R_4} \right) \left(\frac{R_1 + R_2}{R_1} \right) \right] v_2 - \left(\frac{R_2}{R_1} \right) v_1,$$

Table 4-3: Summary of op-amp circuits.

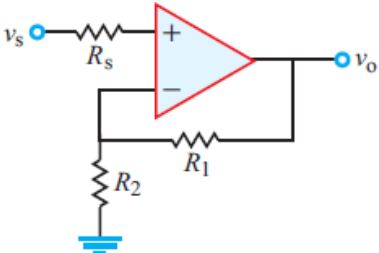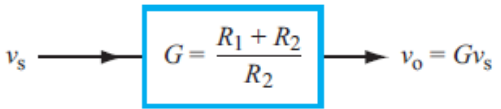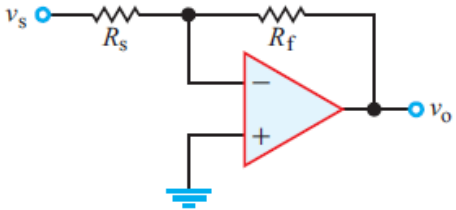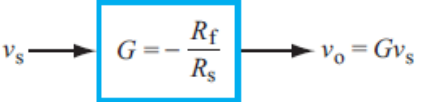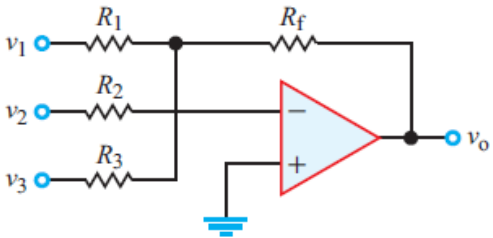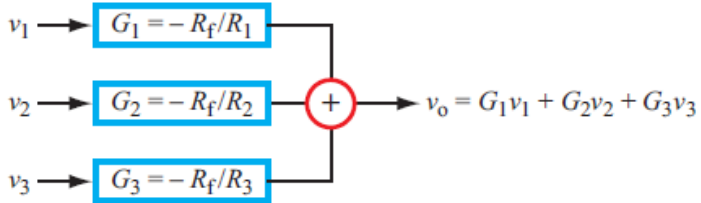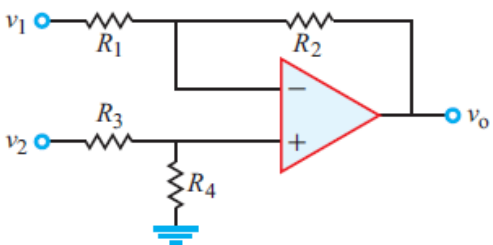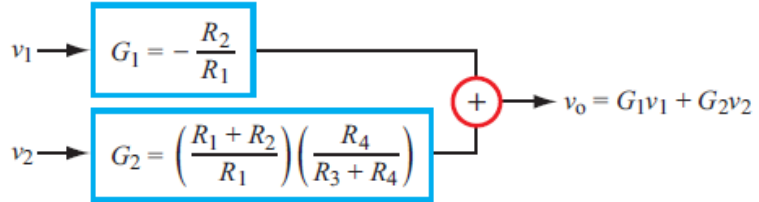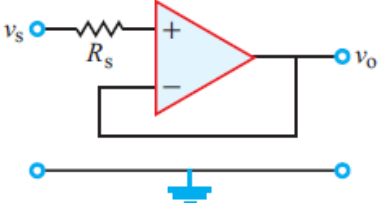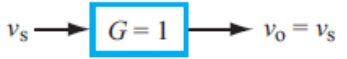Op-Amp Circuit	Block Diagram
 <p>Noninverting Amp (v_o independent of R_s)</p>	 $G = \frac{R_1 + R_2}{R_2} \rightarrow v_o = G v_s$
 <p>Inverting Amp</p>	 $G = -\frac{R_f}{R_s} \rightarrow v_o = G v_s$
 <p>Inverting Summer</p>	 $v_o = G_1 v_1 + G_2 v_2 + G_3 v_3$
 <p>Subtracting Amp</p>	 $v_o = G_1 v_1 + G_2 v_2$
 <p>Voltage Follower (v_o independent of R_s)</p>	 $G = 1 \rightarrow v_o = v_s$

Example 1

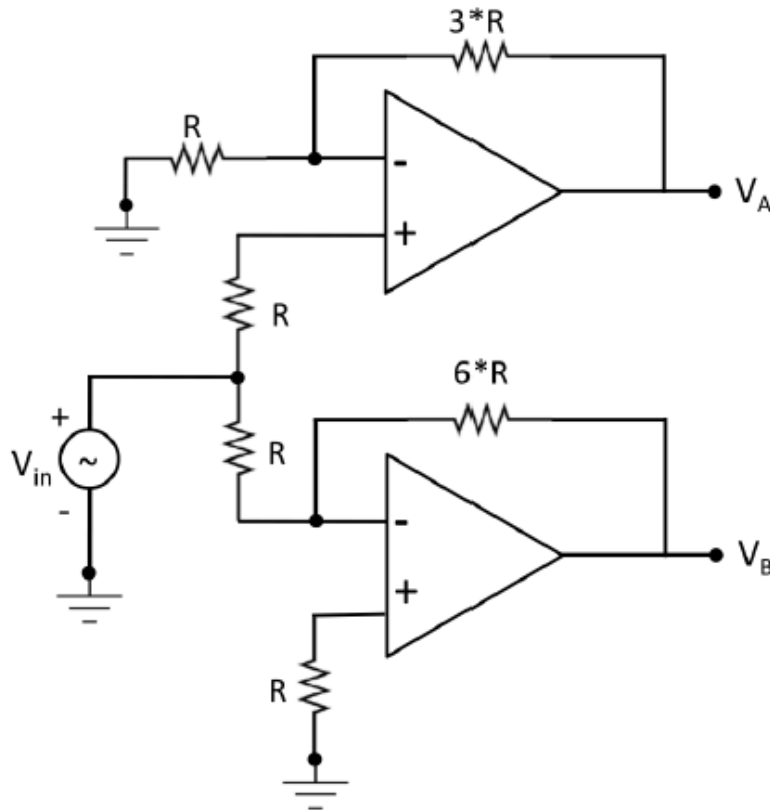


$$\frac{V_A}{V_{in}} = \frac{R + 3R}{R} = 4$$

$$\frac{V_B}{V_{in}} = -\frac{6R}{R} = -6$$

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{V_A - V_B}{V_{in}} \\ &= 4 - (-6) = 10 \end{aligned}$$

1. Find V_A as a function of V_{in} and all resistor values.
2. Repeat for V_B .
3. If we define $V_{out} = V_A - V_B$, what is the gain, V_{out}/V_{in} ?


Example 2

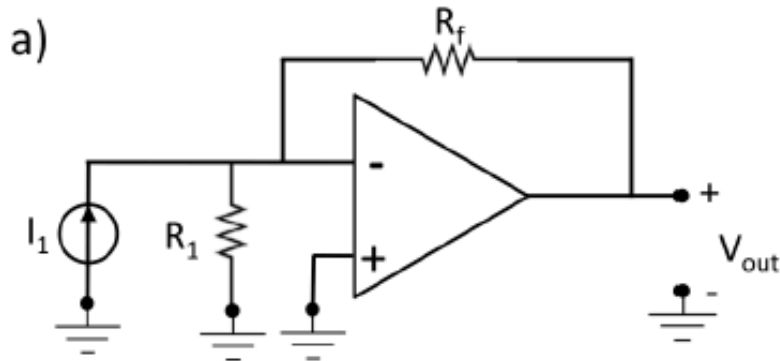

$$\frac{V_{out}}{I_1} = -R_f$$

- ▶ For the circuit (a) above, find V_{out} in terms of R_1 , R_f , I_1 , and I_2 .
Hint: Can we use Thevenin and Norton equivalent circuits?


Example 3

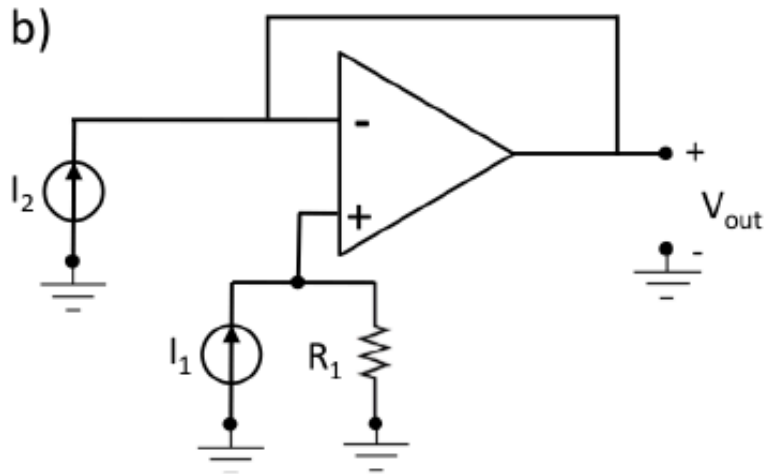

$$\frac{V_{out}}{I_1} = R_1$$

- ▶ For the circuit (b) above, find V_{out} in terms of R_1 , R_f , I_1 , and I_2 . Hint: Can we use Thevenin and Norton equivalent circuits?

Example 4

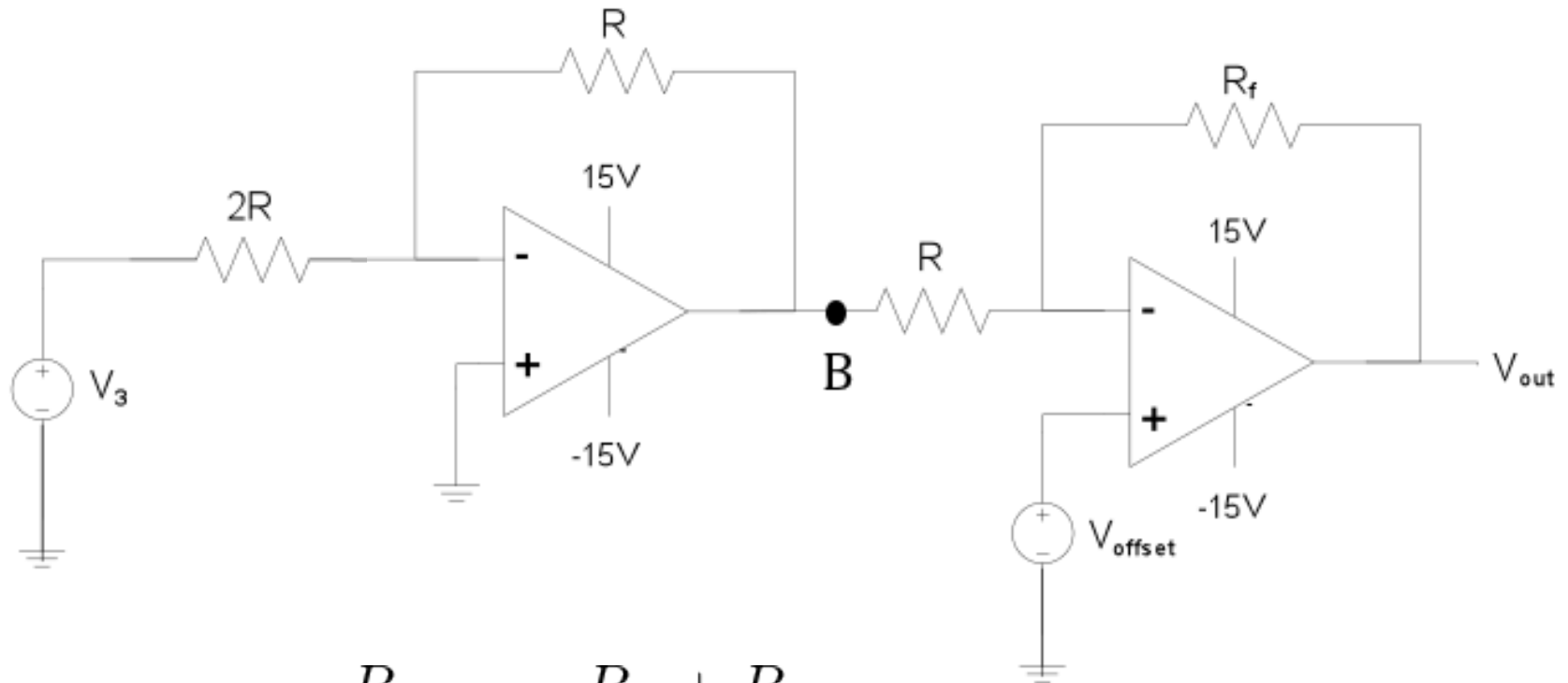


$$V_{\text{out}} = \frac{R_f}{2R} V_3 + \frac{R_f + R}{R} V_{\text{offset}}$$

- Find V_{out} in terms of V_3 , R , R_f , and V_{offset} .


Last example
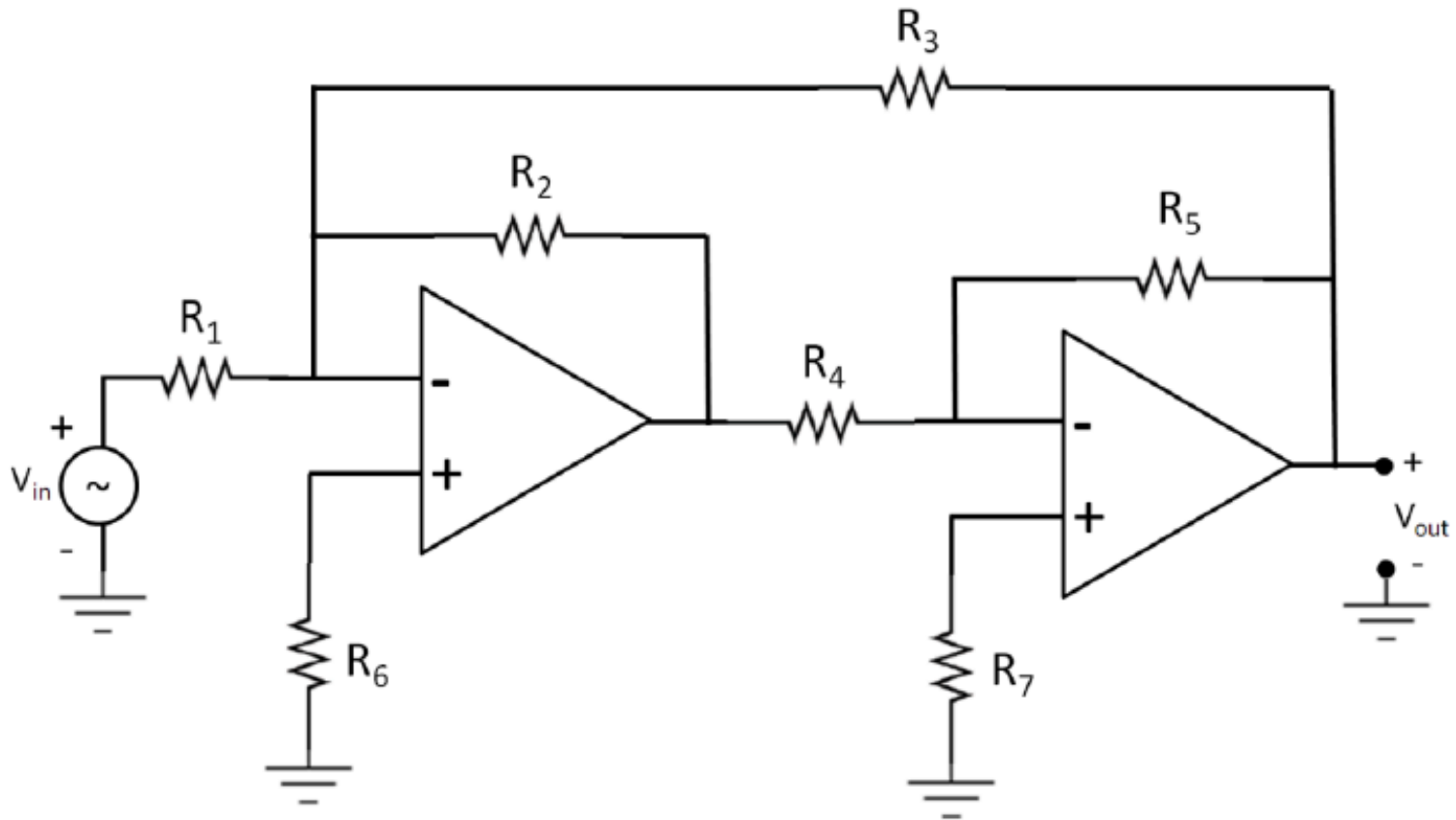
$$\frac{V_{out}}{V_{in}} = \frac{R_2 R_3 R_5}{R_1 R_3 R_4 - R_1 R_2 R_5}$$



- Find V_{out}/V_{in} in terms of $R_1 \sim R_7$.

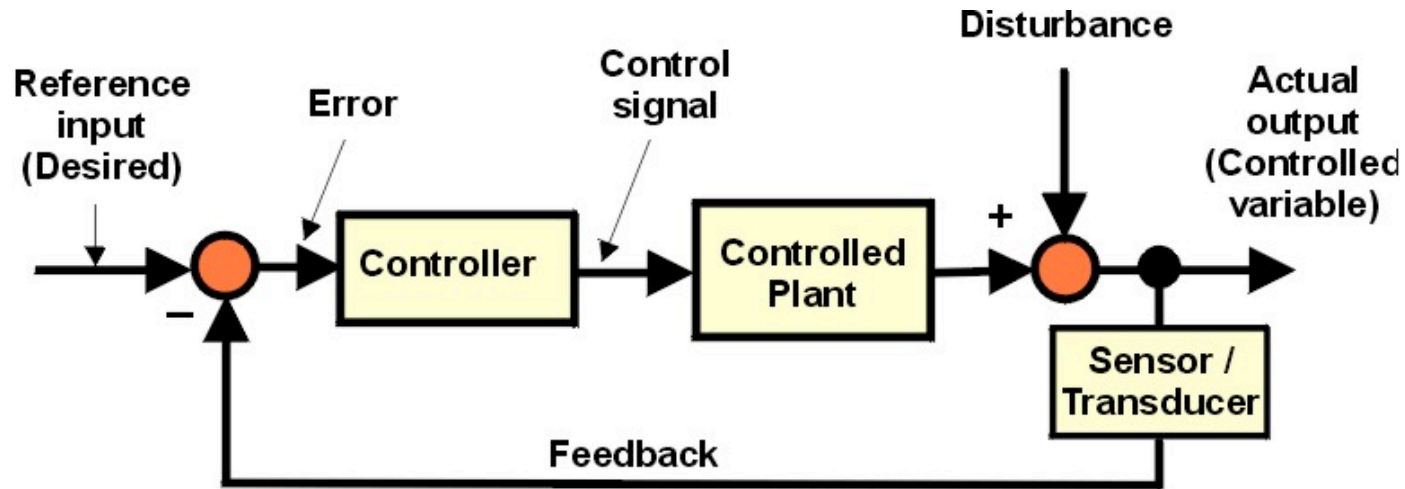Feedback: A general discussion (basics of control theory)



- ▶ **Feedback:** Used to provide a desired output in spite of fluctuations, disturbances, nonlinearity, etc. in the system
- ▶ **The main idea:** The result of an action is fed back to the input and compared to the desired outcome.
- ▶ The principles of feedback are widespread, and can be found in many disciplines:
 - Robotics, electrical and mechanical engineering, manufacturing plants, navigation systems, ecology (wolves and rabbits), business & economics, social systems (health care), and many many more