

# CHAPTER

## Operational Amplifiers


### Contents

- Overview, 151
- 4-1 Op-Amp Characteristics, 151
- TB6 Display Technologies, 155
- 4-2 Negative Feedback, 160
- 4-3 Ideal Op-Amp Model, 161
- 4-4 Inverting Amplifier, 163
- 4-5 Summing Amplifier, 165
- 4-6 Difference Amplifier, 167
- 4-7 Voltage Follower, 168
- 4-8 Op-Amp Signal-Processing Circuits, 169
- 4-9 Instrumentation Amplifier, 174
- 4-10 Digital-to-Analog Converters (DAC), 176
- 4-11 The MOSFET as a Voltage-Controlled Current Source, 179
- TB7 Computer Memory Circuits, 184
- 4-12 Application Note: Neural Probes, 187
- 4-13 Multisim Analysis, 188
- Chapter 4 Summary, 193
- Problems, 193
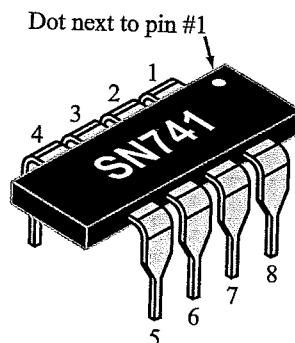
### Objectives

Learn to:

- Describe the basic properties of an op amp and state the constraints of the ideal op-amp model.
- Explain the role of negative feedback and the tradeoff between circuit gain and dynamic range.
- Analyze and design inverting amplifiers, summing amplifiers, difference amplifiers, and voltage followers.



The introduction of the IC *operational amplifier* in the 1960s has led to the development of a wide array of *signal processing circuits*, enabling the creation of an ever-increasing number of *electronic applications*.

- Combine multiple op-amp circuits together to perform signal processing operations.
- Analyze and design high-gain, high-sensitivity instrumentation amplifiers.
- Design an  $n$ -bit digital-to-analog converter.
- Use the MOSFET in analog and digital circuits.
- Apply Multisim to analyze and simulate circuits that include op amps.

### 4-1. OP-AM

#### Overview

Since its first introduction, the *operational amplifier* has become a workhorse of electronic design. It is used in a wide variety of applications, including signal processing, data conversion, and control systems. The *operational amplifier* is a type of *integrated circuit* that can be configured to perform a wide range of functions, including *amplification*, *summation*, *integration*, and *differentiation*. It is a *high-gain* device that can be used to *amplify* signals, *sum* signals, *integrate* signals, and *differentiate* signals. It is a *high-gain* device that can be used to *amplify* signals, *sum* signals, *integrate* signals, and *differentiate* signals.

#### 4-1 Op

The internal  $\epsilon$  interconnects are fabricated on the same chip, however, an

## Overview

Since its first realization by Bob Widlar in 1963 and then its introduction by Fairchild Semiconductor in 1968, the *operational amplifier*, or *op amp* for short, has become the workhorse of many signal-processing circuits. It acquired the adjective *operational* because it is a versatile device capable not only of amplifying a signal but also inverting it (reversing its polarity), integrating it, or differentiating it. When multiple signals are connected to its input, the op amp can perform additional mathematical operations—including addition and subtraction. Consequently, op-amp circuits often are cascaded together in various arrangements to support a variety of different applications. In this chapter, we will explore several op-amp circuit configurations, including amplifiers, summers, voltage followers, and digital-to-analog converters.

## 4-1 Op-Amp Characteristics

The internal architecture of an op-amp circuit consists of many interconnected transistors, diodes, resistors and capacitors—all fabricated on a chip of silicon. Despite its internal complexity, however, an op amp can be modeled in terms of a relatively


simple equivalent circuit that exhibits a linear input-output response. This equivalence allows us to apply the tools we developed in the preceding chapters to analyze (as well as design) a large array of op-amp circuits and to do so with relative ease.

### 4-1.1 Nomenclature


Commercially available op amps are fabricated in encapsulated packages of various shapes. A typical example is the eight-pin DIP configuration shown in Fig. 4-1(a) [DIP stands for dual-in-line package]. The pin diagram for the op amp is shown in Fig. 4-1(b), and its circuit symbol (the triangle) is displayed in Fig. 4-1(c). Of the eight pins (terminals) only five need to be connected to an outside circuit, namely:
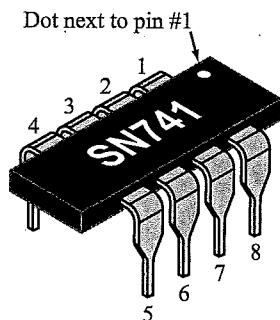
#### Op-Amp Pin Designation


- Pin 2 inverting (or *negative*) input voltage,  $v_n$
- Pin 3 noninverting (or *positive*) input voltage,  $v_p$
- Pin 4 negative (−) terminal of power supply  $V_{cc}$
- Pin 7 positive (+) terminal of power supply  $V_{cc}$
- Pin 6 output voltage,  $v_o$




(a) Typical op-amp package

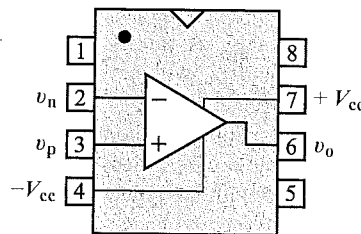

(b) Pin diagram

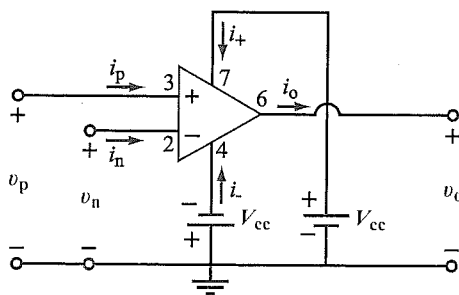

(c) Complete circuit diagram

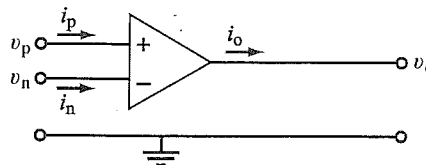

(d) Op-amp diagram without showing  $V_{cc}$  sources explicitly

Figure 4-1: Operational amplifier.

The op amp has two input voltage terminals ( $v_p$  and  $v_n$ ) and one output voltage terminal ( $v_o$ ).

► The terms *noninverting* and *inverting* are associated with the property of the op amp that its output voltage  $v_o$  is directly proportional to both the noninverting input voltage  $v_p$  and the negative of the inverting input voltage  $v_n$ . ◀

Kirchhoff's current law applies to any volume of space, including an op amp. Hence, for the five terminals connected to the op amp, KCL mandates that

$$i_o = i_p + i_n + i_+ + i_-, \quad (4.1)$$

where  $i_p$ ,  $i_n$ , and  $i_o$  may be constant (dc) or time-varying currents. Currents  $i_+$  and  $i_-$  are dc currents generated by the dc power supply  $V_{cc}$ .

► From here on forward, we will ignore the pins connected to  $V_{cc}$  when we draw circuit diagrams involving op amps, because so long as the op amp is operated in its linear region,  $V_{cc}$  will have no bearing on the operation of the circuit. ◀

Hence, in the future, the op-amp triangle usually will be drawn with only three terminals, as shown in Fig. 4-1(d). Moreover, voltages  $v_p$ ,  $v_n$ , and  $v_o$  will be defined relative to a common reference or ground. The (+) and (−) labels printed on the op-amp triangle simply denote the noninverting and inverting pins of the op amp not the polarities of  $v_p$  or  $v_n$ .

Ignoring the pins associated with the power-supply voltage  $V_{cc}$  does not mean we can ignore currents  $i_+$  and  $i_-$ . To avoid making the mistake of writing a KCL equation on the basis of the simplified diagram given in Fig. 4-1(d), we explicitly state that fact by writing

$$i_o \neq i_p + i_n. \quad (4.2)$$

#### 4-1.2 Transfer Characteristics

The plot shown in Fig. 4-2, which depicts the input-output voltage-transfer characteristic of the op amp, is divided into three regions of operation, denoted the *negative saturation*, *linear*, and *positive saturation* regions. In the linear region, the output voltage  $v_o$  is related to the input voltages  $v_p$  and  $v_n$  by

$$v_o = A(v_p - v_n), \quad (4.3)$$

where  $A$  is called the *op-amp gain*, or the *open-loop gain*. Strictly speaking, this relationship is valid only when the op

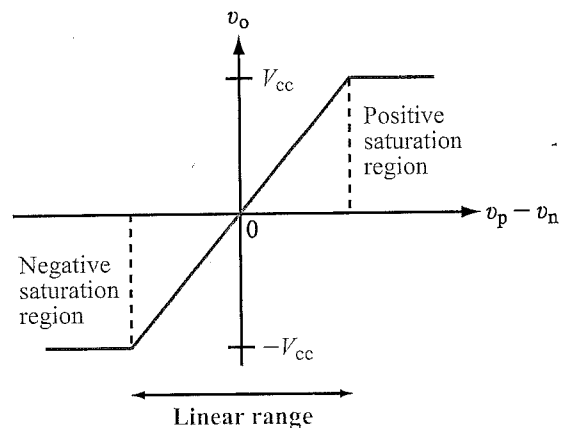


Figure 4-2: Op-amp transfer characteristics. The linear range extends between  $v_o = -V_{cc}$  and  $+V_{cc}$ .

amp is not connected to an external circuit on the output side (open loop), but as will become clearer in future sections, it continues to hold (approximately) if the output circuit satisfies certain conditions. The open-loop gain is specific to the op-amp device itself, in contrast with the *circuit gain* or *closed-loop gain*,  $G$ , which defines the gain of the entire circuit. Thus, if  $v_s$  is the signal voltage of the circuit connected at the input side of the op-amp circuit (Fig. 4-3), and  $v_L$  is the voltage across the load connected at its output side, then

$$v_L = Gv_s. \quad (4.4)$$

According to Eq. (4.3),  $v_o$  is related linearly to the difference between  $v_p$  and  $v_n$  or to either one of them if the other is held constant. Excluding circuits that contain magnetically coupled transformers, in a regular circuit, no voltage can exceed the net voltage level of the power supply.

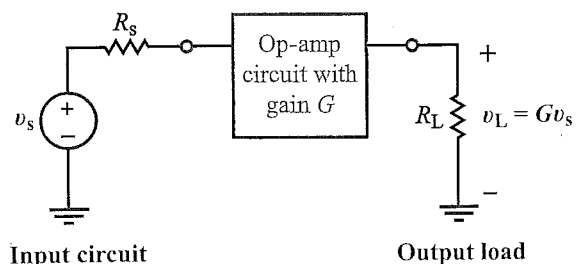



Figure 4-3: Circuit gain  $G$  is the ratio of the output voltage  $v_L$  to the signal input voltage  $v_s$ .

**Table 4-1:** Characteristics and typical ranges of op-amp parameters. The rightmost column represents the values assumed by the ideal op-amp model.

Op-Amp Characteristics	Parameter	Typical Range	Ideal Op Amp
• Linear input-output response	Open-loop gain $A$	$10^4$ to $10^8$ (V/V)	$\infty$
• High input resistance	Input resistance $R_i$	$10^6$ to $10^{13} \Omega$	$\infty \Omega$
• Low output resistance	Output resistance $R_o$	1 to $100 \Omega$	$0 \Omega$
• Very high gain	Supply voltage $V_{cc}$	5 to 24 V	As specified by manufacturer

► The maximum value that  $v_o$  can attain is  $|V_{cc}|$ . The op amp goes into a saturation mode if  $|A(v_p - v_n)| > |V_{cc}|$ , which can occur on both the negative and positive sides of the linear region. ◀

As we will discuss shortly, the op-amp gain  $A$  is typically on the order of  $10^5$  or greater, and the supply voltage is on the order of volts or tens of volts. In the linear region,  $v_o$  is bounded between  $-V_{cc}$  and  $+V_{cc}$ , which means that  $(v_p - v_n)$  is bounded between  $-V_{cc}/A$  and  $+V_{cc}/A$ . For  $V_{cc} = 10$  V and  $A = 10^6$ , the operating range of  $(v_p - v_n)$  is  $-10 \mu\text{V}$  to  $+10 \mu\text{V}$ . It is important to keep this in mind as we deal with circuits containing operational amplifiers.

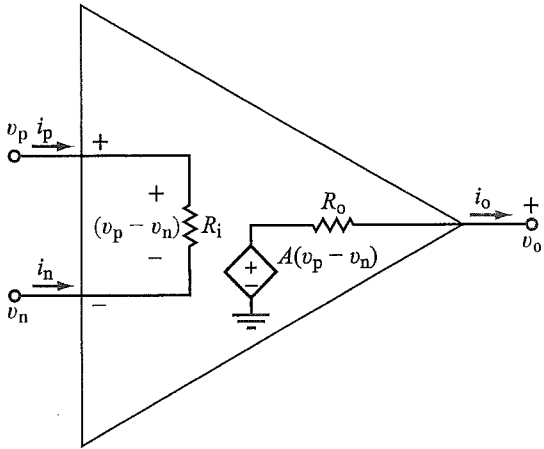

**Figure 4-4:** Equivalent circuit model for an op amp operating in the linear range. Voltages  $v_p$ ,  $v_n$ , and  $v_o$  are referenced to ground.

4-1.3 Equivalent-Circuit Model

When operated in its linear region, the op-amp input-output behavior can be modeled in terms of the equivalent circuit shown in Fig. 4-4. The equivalent circuit consists of a voltage-controlled voltage source of magnitude  $A(v_p - v_n)$ , an input resistance  $R_i$ , and an output resistance  $R_o$ . Table 4-1 lists the typical range of values that each of these op-amp parameters may assume. Based on these values, we note that an op amp is characterized by:

- (1) *High input resistance  $R_i$ :* at least  $1 \text{ M}\Omega$ , which is highly desirable from the standpoint of voltage transfer from an input circuit (as discussed previously in Section 3-6).
- (2) *Low output resistance  $R_o$ :* which is desirable from the standpoint of transferring the op-amp's output voltage to a load circuit.
- (3) *High voltage gain  $A$ :* which is the key, as we will see later, to allowing us to further simplify the equivalent circuit into an "ideal" op-amp model with infinite gain.

**Example 4-1: Noninverting Amplifier**

The circuit shown in Fig. 4-5 uses an op amp to amplify the input signal voltage  $v_s$ . Obtain an expression for the circuit gain  $G = v_o/v_s$ , and then evaluate it for  $V_{cc} = 10$  V,  $A = 10^6$ ,  $R_i = 10 \text{ M}\Omega$ ,  $R_o = 10 \Omega$ ,  $R_1 = 80 \text{ k}\Omega$ , and  $R_2 = 20 \text{ k}\Omega$ .

**Solution:** For reference purposes, we label the output as terminal  $a$  and the node from which a current is fed back into the op amp as terminal  $b$ . The current  $i_3$  flowing from terminal  $b$  to terminal  $a$  is the same as the current  $i_4$  flowing from terminal  $a$  towards  $R_o$ . When expressed in terms of node voltages, the equality  $i_3 = i_4$  gives

$$\frac{v_n - v_o}{R_1} = \frac{v_o - A(v_p - v_n)}{R_o} \quad (\text{node } a). \quad (4.5)$$

At node  $b$ , KCL gives  $i_1 + i_2 + i_3 = 0$  or

$$\frac{v_n - v_p}{R_1} + \frac{v_n}{R_2} + \frac{v_n - v_o}{R_1} = 0. \quad (\text{node } b). \quad (4.6)$$

Additionally,

$$v_p = v_s. \quad (4.7)$$

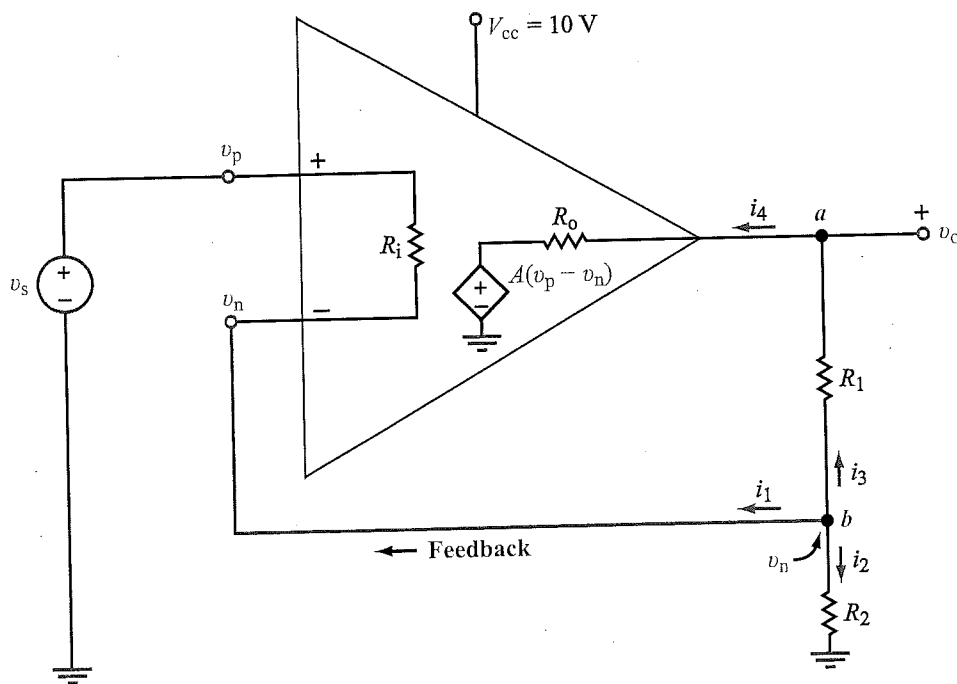


Figure 4-5: Noninverting amplifier circuit of Example 4-1.

Solution of these simultaneous equations leads to the following expression for the circuit gain  $G$ :

$$G = \frac{v_o}{v_s} = \frac{[AR_i(R_1 + R_2) + R_2R_o]}{AR_2R_1 + R_o(R_2 + R_1) + R_1R_2 + R_i(R_1 + R_2)} \quad (4.8)$$

For  $V_{cc} = 10 \text{ V}$ ,  $A = 10^6$ ,  $R_i = 10^7 \Omega$ ,  $R_o = 10 \Omega$ ,  $R_1 = 80 \text{ k}\Omega$ , and  $R_2 = 20 \text{ k}\Omega$ , we have

$$G = \frac{v_o}{v_s} = 4.999975 \approx 5.0. \quad (4.9)$$

In the expression for  $G$ , the two parameters  $A$  and  $R_i$  are several orders of magnitude larger than all of the others. Also,  $R_o$  is in series with  $R_1$ , which is 8000 times larger. Hence, we would incur minimal error if we let  $A \rightarrow \infty$ ,  $R_i \rightarrow \infty$ , and  $R_o \rightarrow 0$ , in which case the expression for  $G$  reduces to

$$G \approx \frac{R_1 + R_2}{R_2} \quad (\text{ideal op-amp model}). \quad (4.10)$$

This approximation, based on the ideal op-amp model that will be introduced in Section 4-3, gives

$$G = \frac{80 \text{ k}\Omega + 20 \text{ k}\Omega}{20 \text{ k}\Omega} = 5.$$

**Concept Question 4-1:** How is the linear range of an op amp defined?

**Concept Question 4-2:** What is the difference between the op-amp gain  $A$  and the circuit gain  $G$ ?

**Concept Question 4-3:** An op amp is characterized by three important input-output attributes. What are they?

**Exercise 4-1:** In the circuit of Example 4-1 shown in Fig. 4-5, insert a series resistance  $R_s$  between  $v_s$  and  $v_p$  and then repeat the solution to obtain an expression for  $G$ . Evaluate  $G$  for  $R_s = 10 \Omega$  and use the same values listed in Example 4-1 for the other quantities. What impact does the insertion of  $R_s$  have on the magnitude of  $G$ ?

**Answer:**

$$G = \frac{[A(R_i + R_s)(R_1 + R_2) + R_2R_o]}{[AR_2(R_i + R_s) + R_o(R_2 + R_1 + R_s) + R_1R_2 + (R_i + R_s)(R_1 + R_2)]}$$


$$= 4.999977 \quad (\text{negligible impact}).$$

(See )
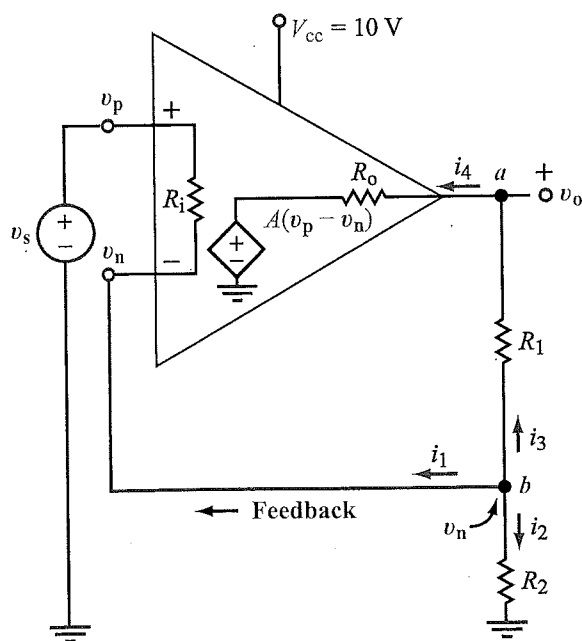
## 4-2 Negative Feedback

Feedback refers to taking a part of the output signal and feeding it back into the input. It is called *positive feedback* if it increases the intensity of the input signal, and it is called *negative feedback* if it decreases it. Positive feedback causes the op amp to saturate, thereby forcing its output voltage  $v_o$  to become equal to its supply voltage  $V_{cc}$ . This behavior is used to advantage in certain types of applications but they are outside the scope of this book. Negative feedback, on the other hand, is an essential ingredient of all of the op-amp circuits covered in this and forthcoming chapters.

Why do op-amp circuits need feedback and why negative feedback specifically? It seems counter-intuitive to want to decrease the input signal when the intent is to amplify it! We will answer this question by examining the circuit of Example 4-1 in some detail. To facilitate the discussion we have reproduced the circuit diagram (into a smaller version) and inserted it in Fig. 4-6(a).



(a)

When we say an op amp has a supply voltage  $V_{cc}$  of 10 V, we actually mean that a positive (10 V) dc voltage source is connected to pin 7 of its package and another, negative ( $-10$  V) source is connected to its pin 4 [Fig. 4-1(b)]. The op-amp circuit cannot generate an output voltage  $v_o$  that exceeds its supply voltage. Hence,  $v_o$  is bounded to  $\pm V_{cc}$  which means

$$|v_o| \leq V_{cc},$$


or equivalently,

$$-V_{cc} \leq v_o \leq V_{cc}. \quad (4.11)$$

Thus, the *linear dynamic range* of  $v_o$  extends from  $-V_{cc}$  to  $+V_{cc}$ .

According to Example 4-1,  $v_o$  is related to the signal voltage  $v_s$  by

$$v_o = Gv_s, \quad (4.12)$$

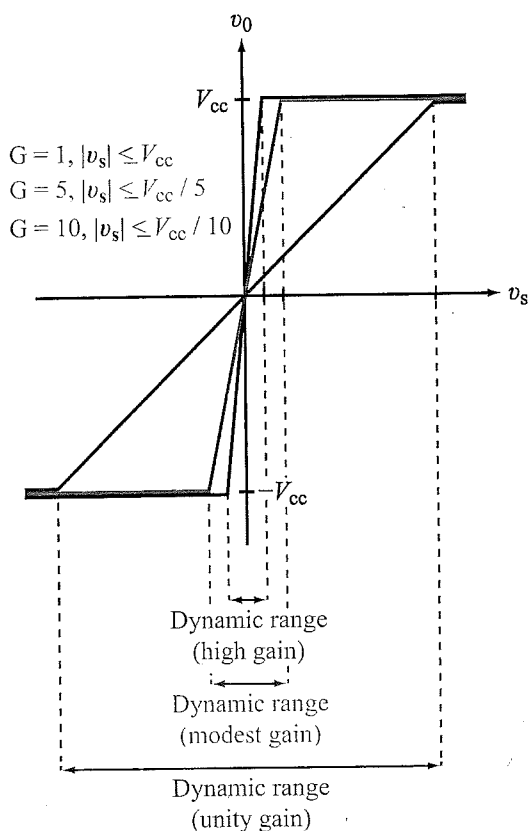

(b) Input-output transfer plots

Figure 4-6: Tradeoff between gain and dynamic range.

with

$$G \approx \frac{R_1 + R_2}{R_2} \quad (4.13)$$

Inserting Eq. (4.12) into Eq. (4.11) gives

$$|Gv_s| \leq V_{cc}, \quad (4.14)$$

or

$$|v_s| \leq \frac{V_{cc}}{G}, \quad (4.15)$$

which states that the linear dynamic range of  $v_s$  is inversely proportional to the circuit gain  $G$ .


(a) **Unity Gain:** If  $R_2 = \infty$  [open circuit between node  $b$  and ground in the circuit of Fig. 4-6(a)], Eq. (4.13) gives  $G \approx 1$ . The corresponding dynamic range of  $v_s$  extends from  $-V_{cc}$  to  $+V_{cc}$ , the same as the output. The input-output transfer plot relating  $v_o$  to  $v_s$  is displayed in green in Fig. 4-6(b).

(b) **Modest Gain:** If we choose  $R_1/R_2 = 4$ , Eq. (4.13) gives  $G = 5$ , and the dynamic range of  $v_s$  now extends from  $-(10/5) = -2\text{ V}$  to  $+2\text{ V}$ . Thus, the gain is higher than the unity-gain case by a factor of 5, but the dynamic range of  $v_s$  is narrower by the same factor.

(c) **Maximum Gain:** If  $R_1$  is removed (replaced with an open circuit between nodes  $a$  and  $b$ ) and  $R_2$  is set equal to zero (short circuit), no feedback will take place in the circuit of Fig. 4-6(a). Use of the exact expression for  $G$  given by Eq. (4.8) leads to  $G = A$ . Since  $A = 10^6$ , the absence of feedback provides a huge gain, but operationally  $v_s$  becomes limited to a very narrow range extending from  $-10\text{ }\mu\text{V}$  to  $+10\text{ }\mu\text{V}$ .

**Exercise 4-2:** To evaluate the tradeoff between the circuit gain  $G$  and the linear dynamic range of  $v_s$ , apply Eq. (4.8) to find the magnitude of  $G$  and then determine the corresponding dynamic range of  $v_s$  for each of the following values of  $R_2$ : 0 (no feedback),  $800\text{ }\Omega$ ,  $8.8\text{ k}\Omega$ ,  $40\text{ k}\Omega$ ,  $80\text{ k}\Omega$ , and  $1\text{ M}\Omega$ . Except for  $R_2$ , all other quantities remain unchanged.

Answer:	$R_2$	$G$	$v_s$ Range
	0	$10^6$	$-10\text{ }\mu\text{V}$ to $+10\text{ }\mu\text{V}$
	$800\text{ }\Omega$	101	$-99\text{ mV}$ to $+99\text{ mV}$
	$8.8\text{ k}\Omega$	10.1	$-0.99\text{ V}$ to $+0.99\text{ V}$
	$40\text{ k}\Omega$	3	$-3.3\text{ V}$ to $+3.3\text{ V}$
	$80\text{ k}\Omega$	2	$-5\text{ V}$ to $+5\text{ V}$
	$1\text{ M}\Omega$	1.08	$-9.26\text{ V}$ to $+9.26\text{ V}$

(See )

### 4-3 Ideal Op-Amp Model

We noted in Section 4-1 that the op amp has a very large input resistance  $R_i$  on the order of  $10^7\text{ }\Omega$ , a relatively small output resistance  $R_o$  on the order of  $1\text{--}100\text{ }\Omega$ , and an open-loop gain  $A \approx 10^6$ . Usually, the series resistances of the input circuit connected to terminals  $v_p$  and  $v_n$  are several orders of magnitude smaller than  $R_i$ . Consequently, not only will very little current flow through the input circuit, but also the voltage drop across the input-circuit resistors will be negligibly small in comparison with the voltage drop across  $R_i$ . These considerations allow us to simplify the equivalent circuit of the op amp by replacing it with the ideal op-amp circuit model shown in Fig. 4-7, in which  $R_i$  has been replaced with an open circuit. An open circuit between terminals  $v_p$  and  $v_n$  implies the following *ideal op-amp current constraint*:

$$i_p = i_n = 0 \quad (\text{ideal op-amp model}). \quad (4.16)$$

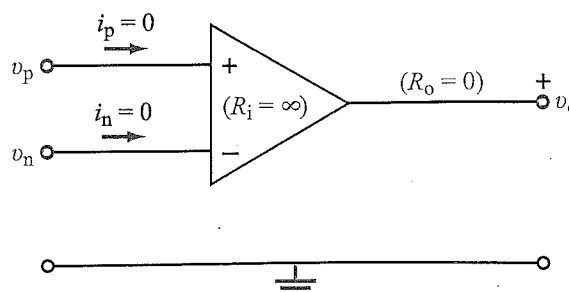


Figure 4-7: Ideal op-amp model.

► Application of negative feedback offers a tradeoff between circuit gain and dynamic range. ◀

**Concept Question 4-4:** Why is negative feedback used in op-amp circuits?

**Concept Question 4-5:** How large is the circuit gain  $G$  in the absence of feedback? How large is it with 100 percent feedback [equivalent to setting  $R_1 = 0$  in the circuit of Fig. 4-6(a)]?

In reality,  $i_p$  and  $i_n$  are very small but not identically zero; for if they were, there would be no amplification through the op amp. Nevertheless, the current condition given by Eq. (4.16) will prove quite useful.

Similarly, at the output side, if the load resistor connected in series with  $R_o$  is several orders of magnitude larger than  $R_o$ , then  $R_o$  can be ignored by setting it equal to zero. Finally, in the ideal op-amp model, the large open-loop gain  $A$  is made infinite—the consequence of which is that

$$v_p - v_n = \frac{v_o}{A} \rightarrow 0 \quad \text{as } A \rightarrow \infty.$$

Hence, we obtain the *ideal op-amp voltage constraint*

$$v_p = v_n \quad (\text{ideal op-amp model}). \quad (4.17)$$

In summary:

► The ideal op-amp model characterizes the op amp in terms of an equivalent circuit in which  $R_i = \infty$ ,  $R_o = 0$ , and  $A = \infty$ . ◀

The operative consequences are given by Eqs. (4.16) and (4.17) and in Table 4-2.


**Table 4-2:** Characteristics of the ideal op-amp model.

Ideal Op Amp		
• Current constraint	$i_p = i_n = 0$	
• Voltage constraint	$v_p = v_n$	
• $A = \infty$	$R_i = \infty$	$R_o = 0$

To illustrate the utility of the ideal op-amp model, let us re-examine the circuit we analyzed earlier in Example 4-1, but we will do so this time using the ideal model. The new circuit, as shown in Fig. 4-8, includes a source resistance  $R_s$ , but because the op amp draws no current ( $i_p = 0$ ), there is no voltage drop across  $R_s$ . Hence,


$$v_p = v_s, \quad (4.18)$$

### Noninverting Amplifier

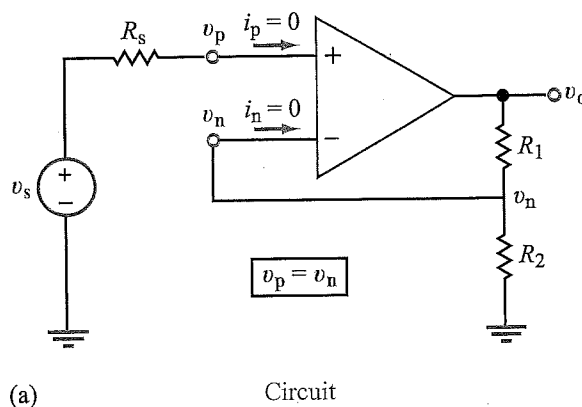

(a)

Circuit

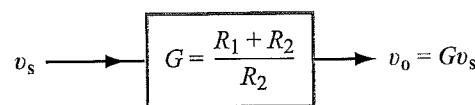

(b)

Block-diagram representation

**Figure 4-8:** Noninverting amplifier circuit: (a) using ideal op-amp model and (b) equivalent block-diagram representation.

and on the output side,  $v_o$  and  $v_n$  are related through voltage division by

$$v_o = \left( \frac{R_1 + R_2}{R_2} \right) v_n. \quad (4.19)$$

Using these two equations, in conjunction with  $v_p = v_n$  (from Eq. (4.17)), we end up with the following result for the circuit gain  $G$ :

$$G = \frac{v_o}{v_s} = \left( \frac{R_1 + R_2}{R_2} \right), \quad (4.20)$$

which is identical with Eq. (4.10).

► From here on forward, we will use the ideal op-amp model exclusively. ◀

The *input resistance* of the noninverting amplifier circuit shown in Fig. 4-8 is the Thévenin resistance of the op-amp circuit as seen by the input source  $v_s$ . Because  $i_p = 0$ , it is easy to show that  $R_{\text{input}} = R_i \approx \infty$ , where  $R_i$  is the input resistance of the op amp (typically on the order of  $10^9 \Omega$ ).



**Concept Question 4-6:** What are the current and voltage constraints of the ideal op amp?

**Concept Question 4-7:** What are the values of the input and output resistances of the ideal op amp?

**Concept Question 4-8:** In the ideal op-amp model,  $R_o$  is set equal to zero. To satisfy such an approximation, does the load resistance need to be much larger or much smaller than  $R_o$ ? Explain.

**Exercise 4-3:** Consider the noninverting amplifier circuit of Fig. 4-8(a) under the conditions of the ideal op-amp model. Assume  $V_{cc} = 10$  V. Determine the value of  $G$  and the corresponding dynamic range of  $v_s$  for each of the following values of  $R_1/R_2$ : 0, 1, 9, 99,  $10^3$ ,  $10^6$ .

Answer:

$R_1/R_2$	$G$	$v_s$ Range
0	1	-10 V to +10 V
1	2	-5 V to +5 V
9	10	-1 V to +1 V
99	100	-0.1 V to +0.1 V
1000	$\sim 1000$	-10 mV to +10 mV (approx.)
$10^6$	$\sim 10^6$	-10 $\mu$ V to +10 $\mu$ V (approx.)

(See 4-9)

## 4-4 Inverting Amplifier

► In an *inverting amplifier* op-amp circuit, the input source is connected to terminal  $v_n$  (instead of to terminal  $v_p$ ) through an *input source resistance*  $R_s$ , and terminal  $v_p$  is connected to ground. ◀

Feedback from the output continues to be applied at  $v_n$  (through a *feedback resistance*  $R_f$ ), as shown in Fig. 4-9. It is called an *inverting amplifier* because (as we will see shortly) the circuit gain  $G$  is negative.


To relate the output voltage  $v_o$  to the input signal voltage  $v_s$ , we start by writing down the node-voltage equation at terminal  $v_n$  as

$$i_1 + i_2 + i_n = 0 \quad (4.21)$$

or


$$\frac{v_n - v_s}{R_s} + \frac{v_n - v_o}{R_f} + i_n = 0. \quad (4.22)$$

### Inverting Amplifier

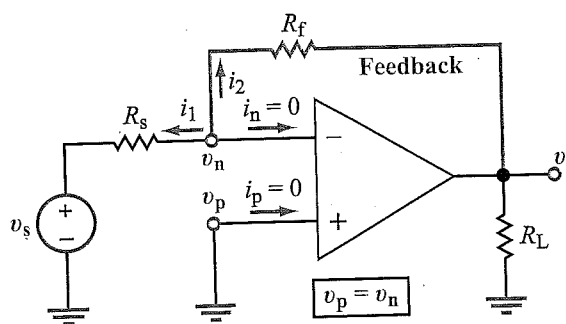

(a)

Circuit

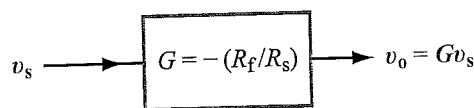

(b)

Block diagram

Figure 4-9: Inverting amplifier circuit and its block-diagram equivalent.

Upon invoking the op-amp current constraint given by Eq. (4.16), namely  $i_n = 0$ , and the voltage constraint  $v_n = v_p$ , as well as recognizing that  $v_p = 0$  (because terminal  $v_p$  is connected to ground), we obtain the relationship

$$v_o = -\left(\frac{R_f}{R_s}\right)v_s. \quad (4.23)$$

The circuit voltage gain of the inverting amplifier therefore is given by

$$G = \frac{v_o}{v_s} = -\left(\frac{R_f}{R_s}\right). \quad (4.24)$$

► In addition to amplifying  $v_s$  by the ratio  $(R_f/R_s)$ , the inverting amplifier also reverses the polarity of  $v_s$ . ◀


►  $v_o$  is independent of the magnitude of the load resistance  $R_L$ , so long as  $R_L$  is much larger than the op-amp output resistance  $R_o$  (which is an implicit assumption of the ideal op-amp model). ◀

Because  $v_n = 0$ , a Thévenin analysis of the circuit in Fig. 4-9(a) would reveal that the *input resistance* of the inverting amplifier circuit (as seen by source  $v_s$ ) is  $R_{\text{input}} = R_{\text{Th}} = R_s$ .


► **Caution:** Under the ideal op-amp model, it is not possible to compute  $i_o$ , the current that flows into the op amp from output terminal  $v_o$ . Hence, it is inappropriate to apply KCL at that terminal. ◀
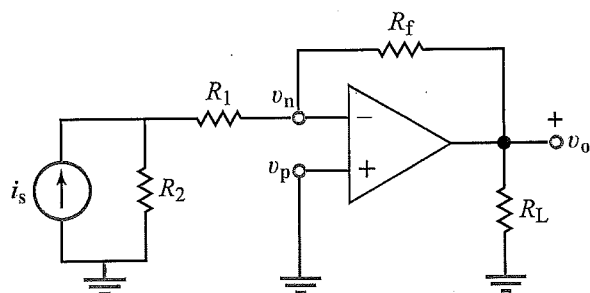
#### Example 4-2: Amplifier with Input Current Source

For the circuit shown in Fig. 4-10(a): (a) obtain an expression for the input-output transfer function  $K_t = v_o/i_s$  and evaluate it for  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$ ,  $R_f = 30 \text{ k}\Omega$ , and  $R_L = 10 \text{ k}\Omega$ ; and (b) determine the linear dynamic range of  $i_s$  if  $V_{\text{cc}} = 20 \text{ V}$ .



(a) Original circuit

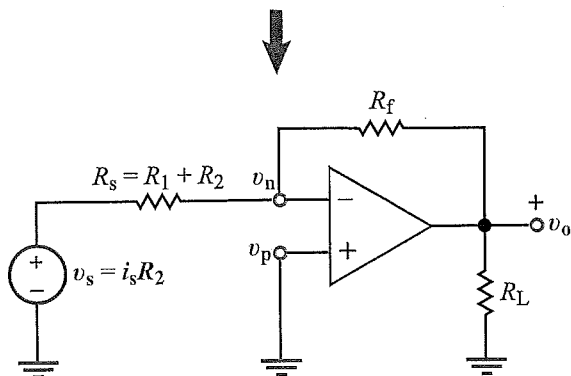

(b) After source transformation

Figure 4-10: Inverting amplifier circuit of Example 4-2.

#### Solution:

(a) Application of the source transformation method converts the combination of  $i_s$  and  $R_2$  into a voltage source  $v_s = i_s R_2$ , in series with a resistance  $R_2$ . Upon combining  $R_2$  in series with  $R_1$ , we obtain the new circuit shown in Fig. 4-10(b), which is identical in form with the inverting amplifier circuit of Fig. 4-9, except that now the source resistance is  $R_s = (R_1 + R_2)$ . Hence, application of Eq. (4.23) gives

$$v_o = -\left(\frac{R_f}{R_1 + R_2}\right)v_s = -\left(\frac{R_f}{R_1 + R_2}\right)R_2 i_s, \quad (4.25)$$

from which we obtain the transfer function

$$K_t = \frac{v_o}{i_s} = -\frac{R_f R_2}{R_1 + R_2}. \quad (4.26)$$

For  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$ , and  $R_f = 30 \text{ k}\Omega$ ,

$$K_t = \frac{v_o}{i_s} = -2 \times 10^4 \quad (\text{V/A}).$$

(b) From the expression for  $K_t$ ,

$$i_s = -\frac{v_o}{2 \times 10^4},$$

and since  $|v_o|$  is bounded by  $V_{\text{cc}} = 20 \text{ V}$ , the linear range for  $i_s$  is bounded by


$$|i_s| = \left| \frac{V_{\text{cc}}}{2 \times 10^4} \right| = \left| \frac{20}{2 \times 10^4} \right| = 1 \text{ mA}.$$

Thus, the linear range of  $i_s$  extends from  $-1 \text{ mA}$  to  $+1 \text{ mA}$ .

**Concept Question 4-9:** How does feedback control the gain of the inverting-amplifier circuit?

**Concept Question 4-10:** The expression given by Eq. (4.24) states that the gain of the inverting amplifier is independent of the magnitude of  $R_L$ . Would the expression remain valid if  $R_L = 0$ ? Explain.

**Exercise 4-4:** The input to an inverting-amplifier circuit consists of  $v_s = 0.2 \text{ V}$  and  $R_s = 10 \Omega$ . If  $V_{\text{cc}} = 12 \text{ V}$ , what is the maximum value that  $R_f$  can assume before saturating the op amp?

**Answer:**  $G_{\text{max}} = -60$ ,  $R_f = 600 \Omega$ . (See )

## 4-5 Summing Amplifier

By connecting multiple sources in parallel at terminal  $v_n$  of the inverting amplifier, the circuit becomes an *adder* (or more precisely a *scaled inverting adder*). After we demonstrate how such a circuit (usually called a *summing amplifier*) works for two input voltages  $v_1$  and  $v_2$ , we will extend it to multiple sources.

For the circuit shown in Fig. 4-11(a), our goal is to relate the output voltage  $v_o$  to  $v_1$  and  $v_2$ . To do so, we apply the source-transformation technique so as to cast the input circuit in the form of a single voltage source  $v_s$  in series with a source resistance  $R_s$ . The steps involved in the transformation are illustrated in Fig. 4-11(b) and (c). Voltage to current transformation gives  $i_{s1} = v_1/R_1$  and  $i_{s2} = v_2/R_2$ , which can be combined together into a single current source as

$$i_s = i_{s1} + i_{s2} = \frac{v_1}{R_1} + \frac{v_2}{R_2} = \frac{v_1 R_2 + v_2 R_1}{R_1 R_2}. \quad (4.27)$$

Similarly, the two parallel resistors add up to

$$R_s = \frac{R_1 R_2}{R_1 + R_2}. \quad (4.28)$$

If we transform  $(i_s, R_s)$  into a voltage source  $(v_s, R_s)$ , we get

$$v_s = i_s R_s = \left( \frac{v_1 R_2 + v_2 R_1}{R_1 R_2} \right) \frac{R_1 R_2}{R_1 + R_2} = \frac{v_1 R_2 + v_2 R_1}{R_1 + R_2}. \quad (4.29)$$

The circuit in Fig. 4-11(c) is identical in form with that of the inverting amplifier of Fig. 4-9. Hence, by applying the input-output voltage relationship given by Eq. (4.23), we have

$$\begin{aligned} v_o &= - \left( \frac{R_f}{R_s} \right) v_s = - \left( \frac{R_f}{\frac{R_1 R_2}{R_1 + R_2}} \right) \left( \frac{v_1 R_2 + v_2 R_1}{R_1 + R_2} \right) \\ &= - \left( \frac{R_f}{R_1} \right) v_1 - \left( \frac{R_f}{R_2} \right) v_2. \end{aligned} \quad (4.30)$$

This expression for  $v_o$  can be written in the form

$$v_o = G_1 v_1 + G_2 v_2, \quad (4.31)$$

where  $G_1 = -(R_f/R_1)$  is the (negative) gain applied to source voltage  $v_1$ , and  $G_2 = -(R_f/R_2)$  is the gain applied to  $v_2$ . Thus:

► The summing amplifier scales  $v_1$  by  $G_1$  and  $v_2$  by  $G_2$  and adds them together. ◀

For the special case where  $R_1 = R_2 = R$ ,

$$v_o = - \left( \frac{R_f}{R} \right) [v_1 + v_2] \quad (\text{equal gain}), \quad (4.32)$$

### Summing Amplifier

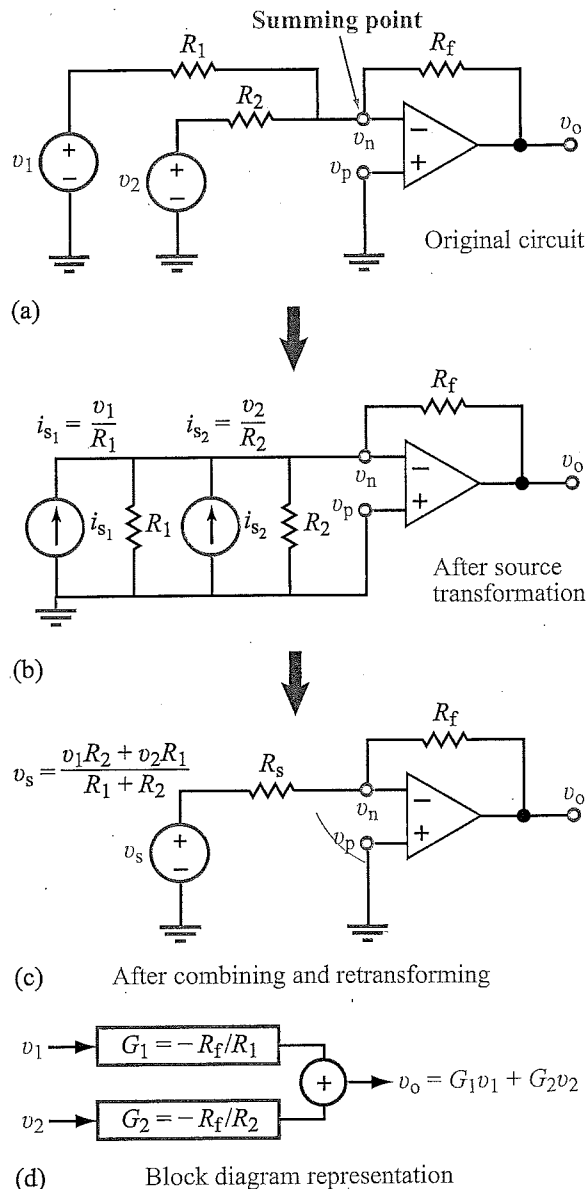
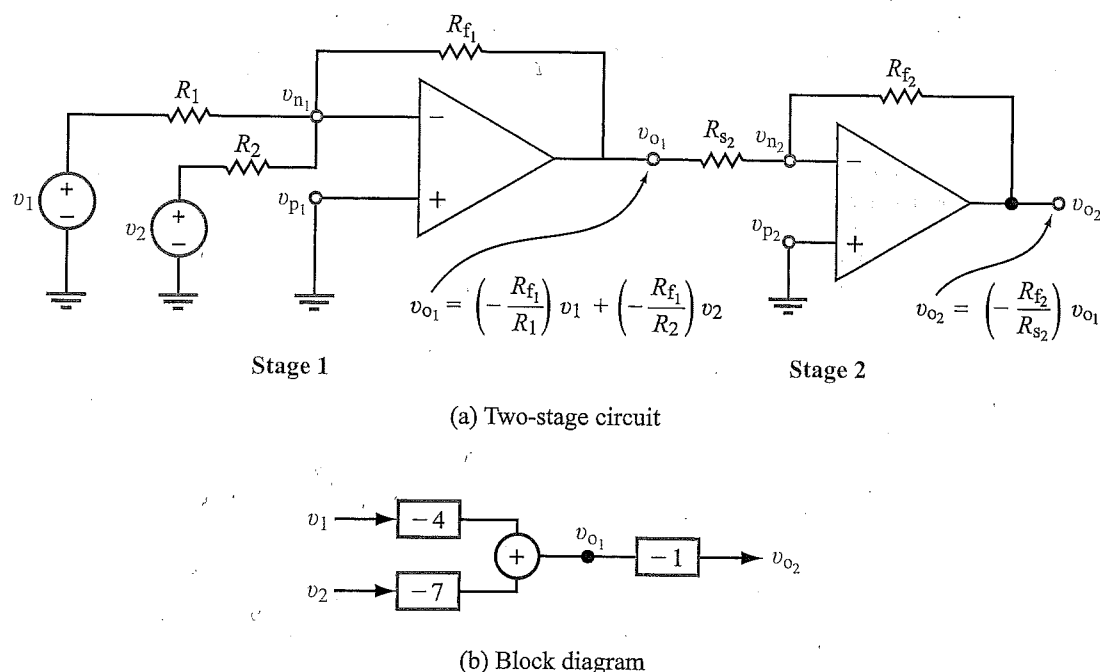


Figure 4-11: Summing amplifier.

and if additionally,  $R_f = R_1 = R_2$ , then  $G_1 = G_2 = -1$ . In this case, the summing amplifier becomes an inverted adder as characterized by

$$v_o = -(v_1 + v_2) \quad (\text{inverted adder}). \quad (4.33)$$

Figure 4-12: Two-stage circuit realization of  $v_o = 4v_1 + 7v_2$ .

Generalizing to the case where the input consists of  $n$  input voltage sources  $v_1$  to  $v_n$  (associated with source resistances  $R_1$  to  $R_n$ , respectively) and all are connected in parallel at the same summing point (terminal  $v_n$ ), the output voltage becomes

$$v_o = \left(-\frac{R_f}{R_1}\right)v_1 + \left(-\frac{R_f}{R_2}\right)v_2 + \cdots + \left(-\frac{R_f}{R_n}\right)v_n \quad (4.34)$$

### Example 4-3: Summing Circuit

Use inverting amplifiers to design a circuit that performs the operation

$$v_o = 4v_1 + 7v_2.$$

**Solution:** The desired circuit has to amplify  $v_1$  by a factor of 4, amplify  $v_2$  by a factor of 7, and add the two together. A summing amplifier can do that, but it also inverts the sum. Hence, we will need to use a two-stage circuit with the first stage providing the desired operation within a “−” sign and then follow it up with an inverting amplifier with a gain of (−1). The two-stage circuit is shown in Fig. 4-12.

For the first stage, we need to select values for  $R_1$ ,  $R_2$ , and  $R_{f1}$  such that

$$\frac{R_{f1}}{R_1} = 4 \quad \text{and} \quad \frac{R_{f1}}{R_2} = 7.$$

Since we have only two constraints, we can satisfy the specified ratios with an infinite number of combinations. Arbitrarily, we choose  $R_{f1} = 56 \text{ k}\Omega$ , which then specifies the other resistors as

$$R_1 = 14 \text{ k}\Omega \quad \text{and} \quad R_2 = 8 \text{ k}\Omega.$$

For the second stage, a gain of (−1) requires that

$$\frac{R_{f2}}{R_{s2}} = 1.$$

Arbitrarily, we choose  $R_{f2} = R_{s2} = 20 \text{ k}\Omega$ .

To perform the summing operation, the solution offered in Example 4-3 employed two inverting amplifier circuits—one to perform an inverted sum, and a second one to provide multiplication by (−1). Alternatively, the same result can be achieved by using a single op amp in a noninverting amplifier circuit, as shown in Fig. 4-13.

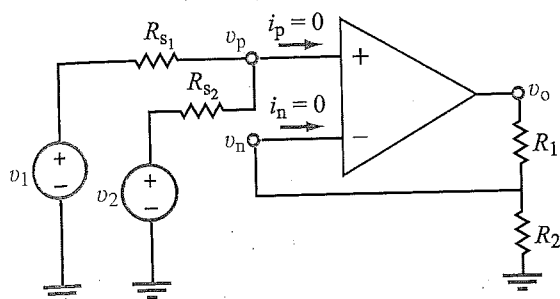


Figure 4-13: Noninverting summer.

From our analysis in Section 4-3, we established that the output voltage  $v_o$  of the noninverting amplifier circuit is related to  $v_p$  by

$$\frac{v_o}{v_p} = G = \frac{R_1 + R_2}{R_2}. \quad (4.35)$$

For the circuit in Fig. 4-13, in view of the ideal op-amp constraint that the op amp draws no current ( $i_p = 0$ ), it is a straightforward task to show that

$$v_p = \frac{v_1 R_{s2} + v_2 R_{s1}}{R_{s1} + R_{s2}}. \quad (4.36)$$

Combining Eqs. (4.35) and (4.36) leads to

$$v_o = G \left[ \left( \frac{R_{s2}}{R_{s2} + R_{s1}} \right) v_1 + \left( \frac{R_{s1}}{R_{s1} + R_{s2}} \right) v_2 \right]. \quad (4.37)$$

To realize a coefficient of 4 for  $v_1$  and a coefficient of 7 for  $v_2$ , it is necessary that

$$\frac{G R_{s2}}{R_{s1} + R_{s2}} = 4$$

and

$$\frac{G R_{s1}}{R_{s1} + R_{s2}} = 7.$$

A possible solution that satisfies these two constraints is  $R_{s1} = 7 \text{ k}\Omega$ ,  $R_{s2} = 4 \text{ k}\Omega$ , and  $G = 11$ . Furthermore, the specified value of  $G$  can be satisfied by choosing  $R_1 = 50 \text{ k}\Omega$  and  $R_2 = 5 \text{ k}\Omega$ .


**Concept Question 4-11:** What type of op-amp circuits (inverting, noninverting, and others) might one use to perform the operation  $v_o = G_1 v_1 + G_2 v_2$  with  $G_1$  and  $G_2$  both positive?

**Concept Question 4-12:** What is an inverting adder?

**Exercise 4-5:** The circuit shown in Fig. 4-12(a) is to be used to perform the operation

$$v_o = 3v_1 + 6v_2.$$

If  $R_1 = 1.2 \text{ k}\Omega$ ,  $R_{s2} = 2 \text{ k}\Omega$ , and  $R_{f2} = 4 \text{ k}\Omega$ , select values for  $R_2$  and  $R_{f1}$  so as to realize the desired result.

**Answer:**  $R_{f1} = 1.8 \text{ k}\Omega$ ,  $R_2 = 600 \Omega$ . (See )

## 4-6 Difference Amplifier

When an input signal  $v_2$  is connected to terminal  $v_p$  of a noninverting amplifier circuit, the output is a scaled version of  $v_2$ . A similar outcome is generated by an inverting amplifier circuit when an input voltage  $v_1$  is connected to the op amp's  $v_n$  terminal, except that in addition to scaling  $v_1$  its polarity is reversed as well. The *difference amplifier* circuit combines these two functions to perform *subtraction*.

In the difference-amplifier circuit of Fig. 4-14(a), the input signals are  $v_1$  and  $v_2$ ,  $R_2$  is the feedback resistance,  $R_1$  is the source resistance of  $v_1$ , and resistances  $R_3$  and  $R_4$  serve to control the scaling factor (gain) of  $v_2$ . To obtain an expression that relates the output voltage  $v_o$  to the inputs  $v_1$  and  $v_2$ , we apply KCL at nodes  $v_n$  and  $v_p$ . At  $v_n$ ,  $i_1 + i_2 + i_n = 0$ , which is equivalent to

$$\frac{v_n - v_1}{R_1} + \frac{v_n - v_o}{R_2} + i_n = 0 \quad (\text{node } v_n). \quad (4.38)$$

At  $v_p$ ,  $i_3 + i_4 + i_p = 0$ , or

$$\frac{v_p - v_2}{R_3} + \frac{v_p}{R_4} + i_p = 0 \quad (\text{node } v_p). \quad (4.39)$$


Upon imposing the ideal op-amp constraints  $i_p = i_n = 0$  and  $v_p = v_n$ , we end up with

$$v_o = \left[ \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_1} \right) \right] v_2 - \left( \frac{R_2}{R_1} \right) v_1, \quad (4.40)$$


which can be cast in the form

$$v_o = G_2 v_2 + G_1 v_1, \quad (4.41)$$

### Difference Amplifier

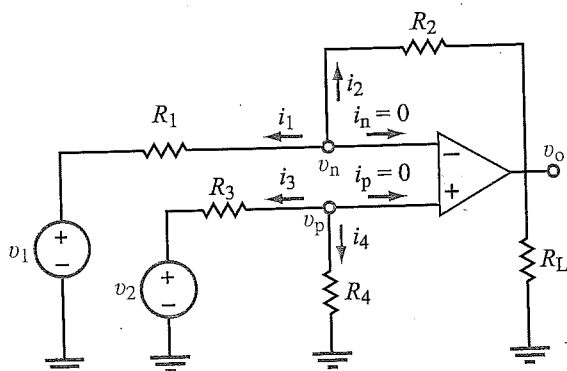

(a) Difference circuit

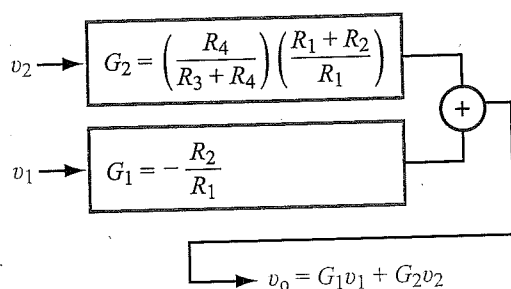

(b) Block diagram

Figure 4-14: Difference-amplifier circuit.

where the scale factors (gains) are given by

$$G_2 = \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_1} \right) \quad (4.42a)$$

and

$$G_1 = - \left( \frac{R_2}{R_1} \right). \quad (4.42b)$$

According to Fig. 4-14(b) which is a block-diagram representation of the difference amplifier circuit:

► The difference amplifier scales  $v_2$  by positive gain  $G_2$ ,  $v_1$  by negative gain  $G_1$  and adds them together. ◀

For the difference amplifier to function as a subtraction circuit with equal gain, its resistors have to be interrelated by

$$R_2 R_3 = R_1 R_4, \quad (4.43)$$

in which case Eq. (4.41) reduces to

$$v_o = \left( \frac{R_2}{R_1} \right) (v_2 - v_1) \quad (\text{equal gain}). \quad (4.44)$$

Exact subtraction with no scaling requires that  $R_1 = R_2$ .

**Exercise 4-6:** The difference-amplifier circuit of Fig. 4-14 is used to realize the operation

$$v_o = (6v_2 - 2)V.$$

Given that  $R_3 = 5 \text{ k}\Omega$ ,  $R_4 = 6 \text{ k}\Omega$ , and  $R_2 = 20 \text{ k}\Omega$ , specify values for  $v_1$  and  $R_1$ .

Answer:  $v_1 = 0.2 \text{ V}$ ,  $R_1 = 2 \text{ k}\Omega$ . (See 4-6)

### 4-7 Voltage Follower

In electronic circuits, we often need to incorporate the functionality of a relatively simple (but important) circuit that serves to insulate the input source from variations in the load resistance  $R_L$ . Such a circuit is called a *voltage follower* or *buffer*. To appreciate the utility of the voltage follower, let us first examine the circuit shown in Fig. 4-15(a). An input circuit represented by its Thévenin equivalent ( $v_s$ ,  $R_s$ ), is connected to a load  $R_L$ . The output voltage is

$$v_o = \frac{v_s R_L}{R_s + R_L} \quad (\text{without voltage follower}), \quad (4.45)$$


which obviously is dependent on both  $R_s$  and  $R_L$ .

In contrast, when the op-amp voltage follower circuit shown in Fig. 4-15(b) is inserted in between the input circuit and the load, the output voltage becomes completely independent of both  $R_s$  and  $R_L$ . Because  $i_p = 0$ , it follows that  $v_p = v_s$ . Furthermore, in view of the op-amp constraint  $v_p = v_n$  and because the output node is connected directly to  $v_n$ , it follows that


$$v_o = v_p = v_s \quad (\text{with voltage follower}), \quad (4.46)$$

and this is true regardless of the values of  $R_s$  and  $R_L$  (excluding  $R_s = \text{open circuit}$  and/or  $R_L = \text{short circuit}$ , either of which would invalidate the entire circuit). Thus:

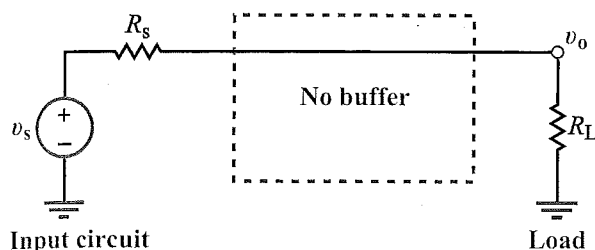► The output of the voltage follower *follows* the input signal while remaining immune to changes in  $R_L$ . ◀



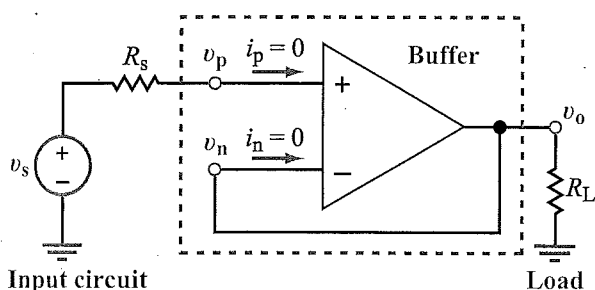(a) Input circuit connected directly to a load



(b) Input circuit separated by a buffer

Figure 4-15: The voltage follower provides no voltage gain ( $v_o = v_s$ ), but it insulates the input circuit from the load.

A circuit that offers this type of protection is often called a *buffer*.

**Concept Question 4-13:** What is the function of a voltage follower, and why is it called a “buffer”?

**Concept Question 4-14:** How much voltage gain is provided by the voltage follower?

**Exercise 4-7:** Express  $v_o$  in terms of  $v_1$ ,  $v_2$ , and  $v_3$  for the circuit in Fig. E4-7.

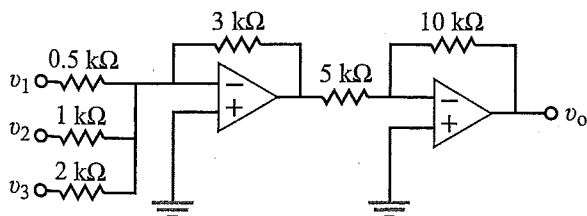



Figure E4-7

**Answer:**  $v_o = 12v_1 + 6v_2 + 3v_3$ . (See )

## 4-8 Op-Amp Signal-Processing Circuits

Table 4-3 provides a summary of the op-amp circuits we have considered thus far, together with their functional characteristics in the form of block-diagram representations. These circuits can be used in various combinations to realize specific signal-processing operations. We note that the input-output transfer functions are independent of the load resistance  $R_L$  that may be connected between the output terminal  $v_o$  and ground. In the case of the noninverting amplifier, the transfer function is also independent of the source resistance  $R_s$ .

► When cascading multiple stages of op-amp circuits in series, care must be exercised to ensure that none of the op amps is driven into saturation by the cumulative gain of the multiple stages. ◀

When analyzing circuits that involve op amps, whether in configurations similar to or different from those we encountered so far in this chapter, the basic rules to remember are as follows:

### Basic Rules of Op-Amp Circuits

- (1) KCL and KVL always apply everywhere in the circuit, but KCL fails at the output node when applying the ideal op-amp model.
- (2) The op amp will operate in the linear range so long as  $|v_o| < |V_{cc}|$ .
- (3) The ideal op-amp model assumes that the source resistance  $R_s$  (connected to terminals  $v_p$  or  $v_n$ ) is much smaller than the op-amp input resistance  $R_i$  (which usually is no less than  $10 \text{ M}\Omega$ ), and the load resistance  $R_L$  is much larger than the op-amp output resistance  $R_o$  (which is on the order of tens of ohms).
- (4) The ideal op-amp constraints are  $i_p = i_n = 0$  and  $v_p = v_n$ .











### Example 4-4: Interesting Op-Amp Circuit

Generate a plot for  $i_L$  at the output side of the circuit shown in Fig. 4-16(a) versus  $v_s$ , covering the full linear range of  $v_s$ .


**Solution:** At node  $v_n$ , KCL gives

$$\frac{v_n}{2k} + \frac{v_n - v_o}{6k} = 0,$$

Table 4-3: Summary of op-amp circuits.

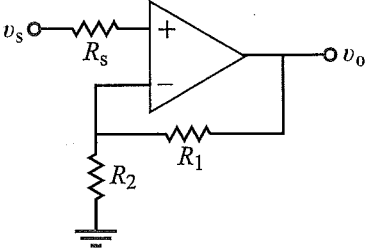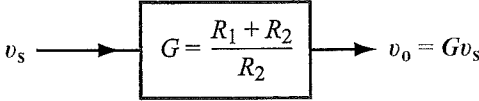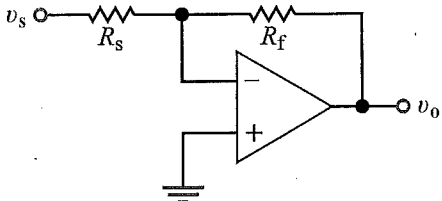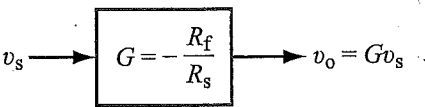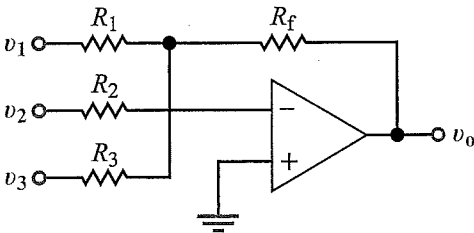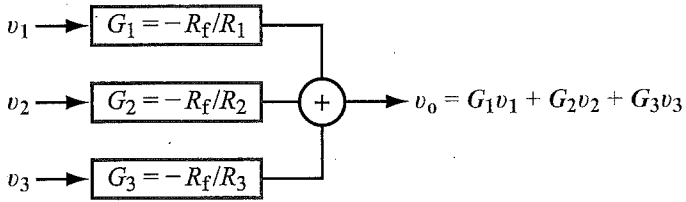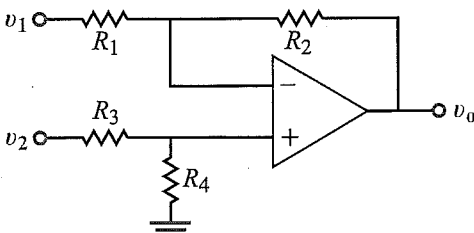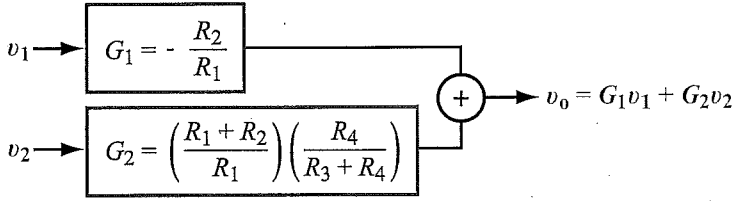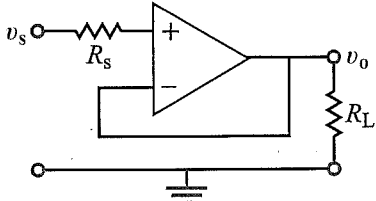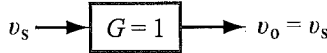Op-Amp Circuit	Block Diagram
 <p>Noninverting Amp (<math>v_o</math> independent of <math>R_s</math>)</p>	 $G = \frac{R_1 + R_2}{R_2}$ $v_o = G v_s$
 <p>Inverting Amp</p>	 $G = -\frac{R_f}{R_s}$ $v_o = G v_s$
 <p>Inverting Summer</p>	 $G_1 = -R_f/R_1$ $G_2 = -R_f/R_2$ $G_3 = -R_f/R_3$ $v_o = G_1 v_1 + G_2 v_2 + G_3 v_3$
 <p>Subtracting Amp</p>	 $G_1 = -\frac{R_2}{R_1}$ $G_2 = \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right)$ $v_o = G_1 v_1 + G_2 v_2$
 <p>Voltage Follower (<math>v_o</math> independent of <math>R_s</math> and <math>R_L</math>)</p>	 $G = 1$ $v_o = v_s$



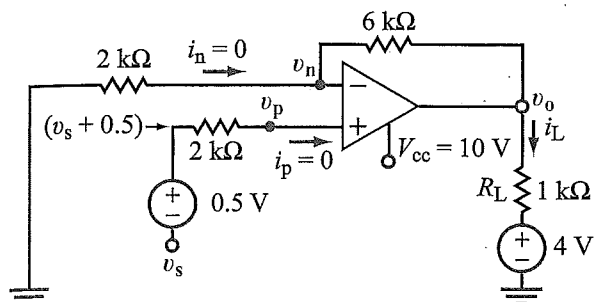

(a) Circuit

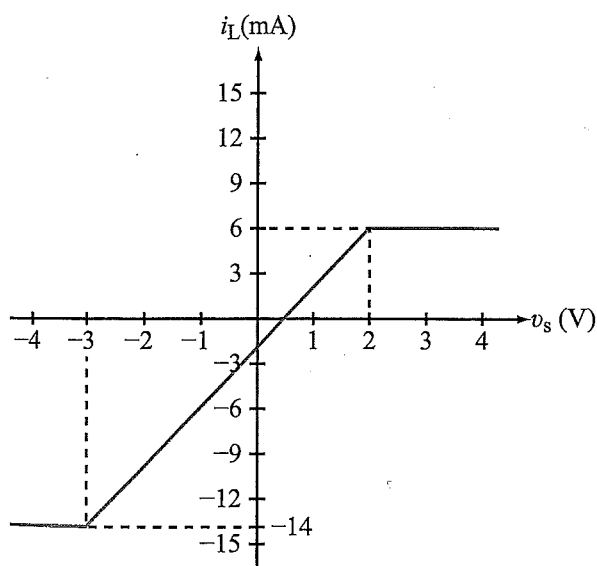
(b)  $i_L - v_s$  transfer plot

Figure 4-16: Circuit for Example 4-4.

which leads to

$$v_o = 4v_n.$$

At node  $v_p$ , KCL gives

$$\frac{v_p - (v_s - 0.5)}{2k} = 0,$$

which leads to

$$v_p = v_s + 0.5.$$

By imposing the op-amp constraint  $v_p = v_n$ , we have

$$v_o = 4v_n = 4(v_s + 0.5) = 4v_s + 2.$$

At the output side,

$$\begin{aligned} i_L &= \frac{v_o - 4}{1k} \\ &= \frac{4v_s + 2 - 4}{1k} = (4v_s - 2) \text{ mA}. \end{aligned}$$

For  $v_o = V_{cc} = 10 \text{ V}$ ,

$$10 = 4v_s + 2, \quad \text{or } v_s = 2 \text{ V},$$

and for  $v_o = -V_{cc} = -10 \text{ V}$ ,

$$-10 = 4v_s + 2, \quad \text{or } v_s = -3 \text{ V}.$$

Hence, linear range of  $v_s$  is

$$-3 \text{ V} \leq v_s \leq 2 \text{ V} \quad (\text{linear range}).$$

Figure 4-16(b) displays a plot of  $i_L$  versus  $v_s$  over the latter's linear range.

#### Example 4-5: Elevation Sensor

A hand-held elevation sensor uses a pair of capacitors separated by a flexible metallic membrane ([Fig. 4-17(a)] to measure the height  $h$  above sea level. The lower chamber in Fig. 4-17(a) is sealed, and its pressure is  $P_0$ , which is the standard atmospheric pressure at sea level. The pressure in the upper chamber, which is open to the outside air, is  $P$ . When at sea level,  $P = P_0$ , so the membrane assumes a flat shape and the two capacitances are equal. Since atmospheric pressure decreases with elevation, a rise in altitude results in a change in the pressure  $P$  in the upper chamber, causing the membrane to bend upwards [Fig. 4-17(b)], thereby changing the capacitances of the two capacitors. The sensor measures a voltage  $v_s$  that is proportional to the change in capacitance.

Based on measurements of  $v_s$  as a function of  $h$ , the data was found to exhibit an approximately linear variation given by

$$v_s = 2 + 0.2h \quad (\text{V}), \quad (4.47)$$

where  $h$  is in km. The sensor is designed to operate over the range  $0 \leq h \leq 10 \text{ km}$ . Design a circuit whose output voltage  $v_o$  (in volts) is an exact indicator of the height  $h$  (in km).

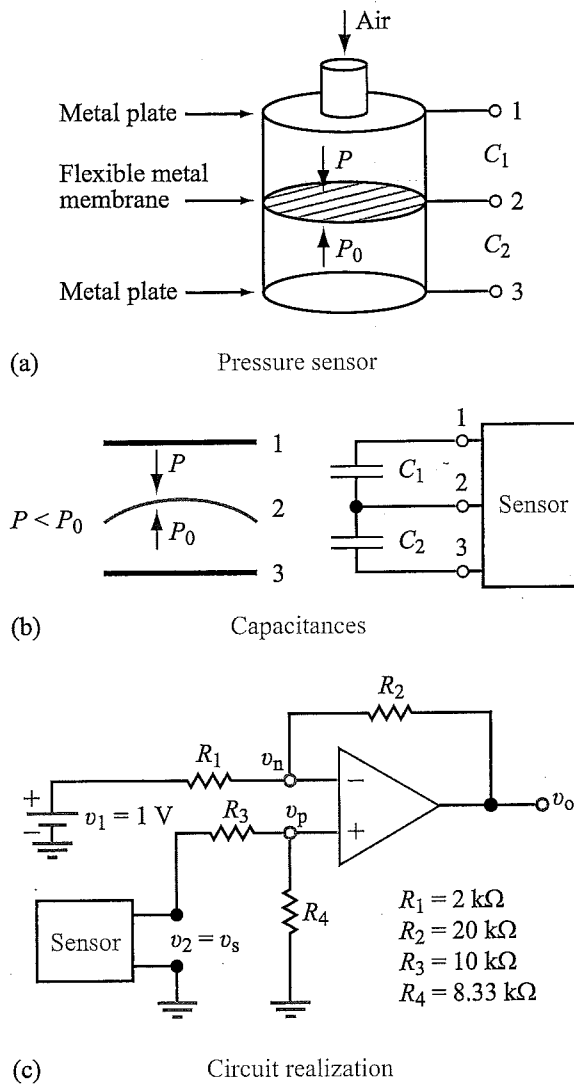


Figure 4-17: Design of a circuit for the pressure sensor of Example 4-5 with  $P_0$  = pressure at sea level and  $P$  = pressure at height  $h$ .

**Solution:** Based on the given information, the sensor voltage  $v_s$  will serve as the input to the circuit we are asked to design, and the output  $v_o$  will represent the height elevation  $h$ . We therefore need a circuit that can perform the operation

$$v_o = h = \frac{1}{0.2} v_s - \frac{2}{0.2} = 5v_s - 10, \quad (4.48)$$

where we have inverted Eq. (4.47) to solve for  $h$  in terms of  $v_s$ . The functional form of Eq. (4.48) indicates that we have only one active (variable) input, namely  $v_s$ , which we need to amplify

by a factor of 5 but also need to subtract 10 V from it. There are multiple circuit configurations that can achieve the desired operation, including the subtractor circuit shown in Fig. 4-17(c). According to Eq. (4.40), the output of the difference amplifier is given by

$$v_o = \left[ \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_1} \right) \right] v_2 - \left( \frac{R_2}{R_1} \right) v_1. \quad (4.49)$$

Equation (4.49) can be made to correspond to Eq. (4.48) if we select the following

- (a)  $v_s = v_2$
- (b)  $v_1$  as a dc voltage source such that  $(R_2/R_1)v_1 = 10$  V, which can be satisfied by arbitrarily selecting  $v_1 = 1$  V and  $(R_2/R_1) = 10$
- (c) values for  $R_1$  through  $R_4$  that simultaneously satisfy the conditions

$$\frac{R_2}{R_1} = 10 \quad \text{and} \quad \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_1} \right) = 5$$

A possible set of values that meets these conditions is

$$\begin{aligned} R_1 &= 2 \text{ k}\Omega, & R_2 &= 20 \text{ k}\Omega, \\ R_3 &= 10 \text{ k}\Omega, & R_4 &= 8.33 \text{ k}\Omega. \end{aligned}$$

Before we conclude the design, we should check to make sure that the op amp will operate in its linear range over the full range of operation of the sensor. According to Eq. (4.47), as  $h$  varies from zero to 10 km,  $v_s$  varies from 2 V to 4 V. The corresponding range of variation of  $v_o$ , from Eq. (4.48), is from zero to 10 V. Hence, we should choose an op amp designed to function with a dc supply voltage  $V_{cc}$  that exceeds 10 V.

#### Example 4-6: Circuit with Multiple Op Amps

Relate the output voltage  $v_o$  to the input voltages  $v_1$  and  $v_2$  of the circuit in Fig. 4-18.

**Solution:** By comparing the circuit connections surrounding the four op amps with those given in Table 4-3, we recognize op amps 1 and 2 as noninverting amplifiers, op amp 3 as an inverting amplifier with a gain of  $-1$  (equal input and feedback resistors  $R_4$ ), and op amp 4 as an inverting summing amplifier with equal gain (same input resistances  $R_6$  at summing point).

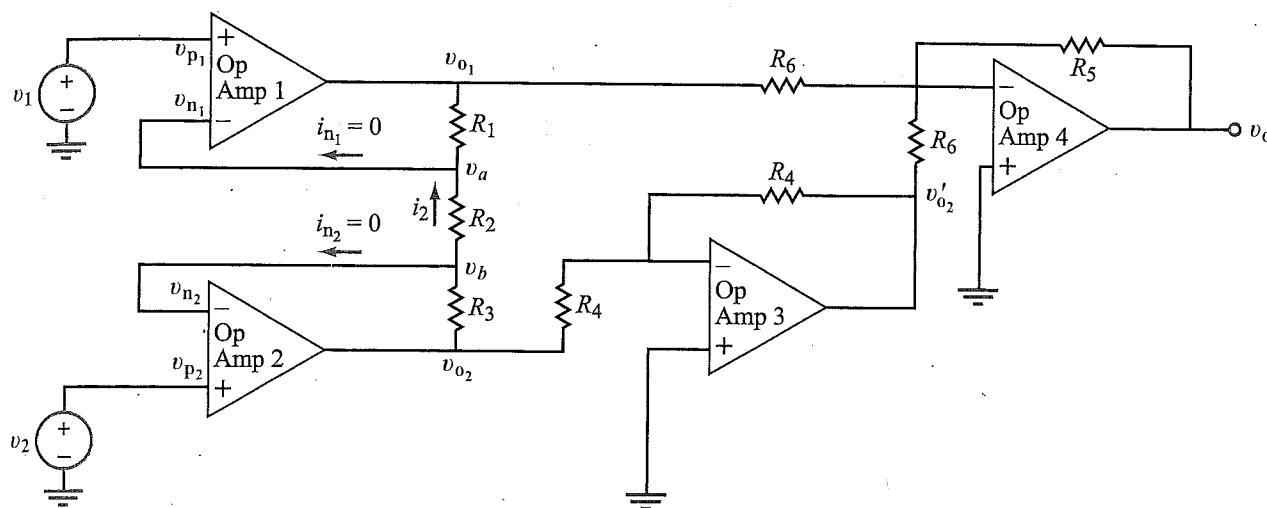


Figure 4-18: Example 4-6.

We start by examining the pair of input op amps. For op amp 1,  $v_{p1} = v_1$  and  $v_{p1} = v_{n1}$  (op amp voltage constraint). Hence,

$$v_a = v_{n1} = v_1.$$

Similarly, for op amp 2,

$$v_b = v_{n2} = v_2.$$

Since  $i_{n1} = i_{n2} = 0$  (op amp current constraint),

$$i_2 = \frac{v_b - v_a}{R_2} = \frac{v_2 - v_1}{R_2},$$

and

$$\begin{aligned} v_{02} - v_{01} &= i_2(R_1 + R_2 + R_3) \\ &= \left( \frac{R_1 + R_2 + R_3}{R_2} \right) (v_2 - v_1). \end{aligned} \quad (4.50)$$

For op amp 3,

$$v'_{02} = -v_{02},$$

and for op amp 4,

$$\begin{aligned} v_o &= -\frac{R_5}{R_6}(v_{01} + v'_{02}) \\ &= -\frac{R_5}{R_6}(v_{01} - v_{02}) \\ &= \frac{R_5}{R_6}(v_{02} - v_{01}) = R_5 \left( \frac{R_1 + R_2 + R_3}{R_6 R_2} \right) (v_2 - v_1). \end{aligned} \quad (4.51)$$

#### Example 4-7: Block-Diagram Representation

Generate a block-diagram representation for the circuit shown in Fig. 4-19(a).

**Solution:** The first op amp is an inverting amplifier with a dc input voltage  $v_1 = 0.42$  V. Its circuit gain  $G_i$  (with the subscript added to denote “inverting amp”) is

$$\begin{aligned} G_i &= -\frac{30K}{10K} \\ &= -3, \end{aligned}$$

and its output is

$$\begin{aligned} v_{01} &= G_i v_1 \\ &= -3(0.42) \\ &= -1.26 \text{ V}. \end{aligned}$$

The second op amp is a difference amplifier. Using Table 4-3, the gains of its positive and negative channels are

$$\begin{aligned} G_2 &= \left( \frac{R_4}{R_3 + R_4} \right) \left( \frac{R_1 + R_2}{R_1} \right) \\ &= \left( \frac{2K}{1K + 2K} \right) \left( \frac{10K + 20K}{10K} \right) \\ &= 2 \end{aligned}$$

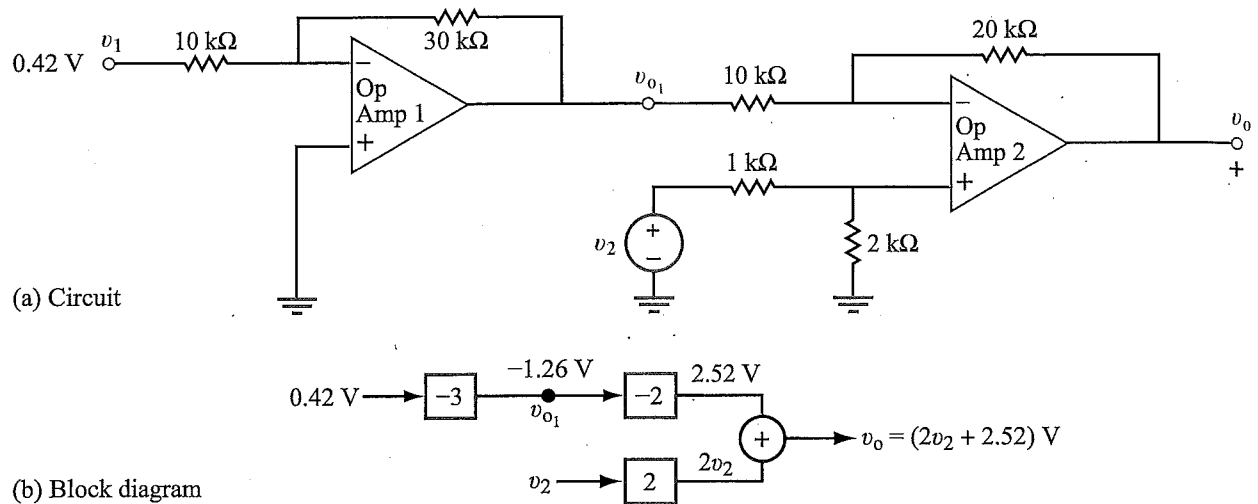


Figure 4-19: Block-diagram representation (Example 4-7).

and

$$\begin{aligned}
 G_1 &= -\frac{R_2}{R_1} \\
 &= -\frac{20K}{10K} \\
 &= -2.
 \end{aligned}$$

Hence,

$$\begin{aligned}
 v_o &= G_2 v_2 + G_1 v_{o1} \\
 &= 2v_2 - 2(-1.26) \\
 &= (2v_2 + 2.52) \text{ V.}
 \end{aligned}$$

## 4-9 Instrumentation Amplifier

An electric *sensor* is a circuit used to measure a physical quantity, such as distance, motion, temperature, pressure, or humidity. In some applications, the intent is not to measure the magnitude of a certain quantity, but rather to sense small deviations from a nominal value. For example, if the temperature in a room is to be maintained at  $20^\circ\text{C}$ , the functional goal of the temperature sensor is to measure the difference between the room temperature  $T$  and the reference temperature  $T_0 = 20^\circ\text{C}$  and then to activate an air conditioning or heating unit if the deviation exceeds a certain prespecified threshold. Let us assume the threshold is  $0.1^\circ\text{C}$ . Instead of requiring the sensor to be able to measure  $T$  with an absolute accuracy of no less than  $0.1^\circ\text{C}$ , an alternative approach would be to

design the sensor to measure  $\Delta v = v_2 - v_1$ , where  $v_2$  is the voltage output of a thermocouple circuit responding to the room temperature  $T$  and  $v_1$  is the voltage corresponding to what a calibrated thermocouple would measure when  $T_0 = 20^\circ\text{C}$ . Thus, the sensor is designed to measure the deviation of  $T$  from  $T_0$ , rather than  $T$  itself, with an absolute accuracy of no less than  $0.1^\circ\text{C}$ . The advantage of such an approach is that the signal is now  $\Delta v$ , which is more than two orders of magnitude smaller than  $v_2$ . A circuit with a precision of 10 percent is not good enough for measuring  $v_2$ , but it is plenty good for measuring  $\Delta v$ .

► The instrumentation amplifier is suited perfectly for detecting and amplifying a small signal deviation when superimposed on one or the other of two much larger (and otherwise identical) signals. ◀

An instrumentation amplifier consists of three op amps, as shown in Fig. 4-20. The circuit configuration for the first two is the same as the one we examined earlier in connection with Example 4-6. According to Eq. (4.50), the voltage difference between the outputs of op amps 1 and 2 is

$$\begin{aligned}
 v_{o2} - v_{o1} &= \left( \frac{R_1 + R_2 + R_3}{R_2} \right) (v_2 - v_1) \\
 &= G_1 (v_2 - v_1),
 \end{aligned} \tag{4.52}$$

## Instrumentation Amplifier

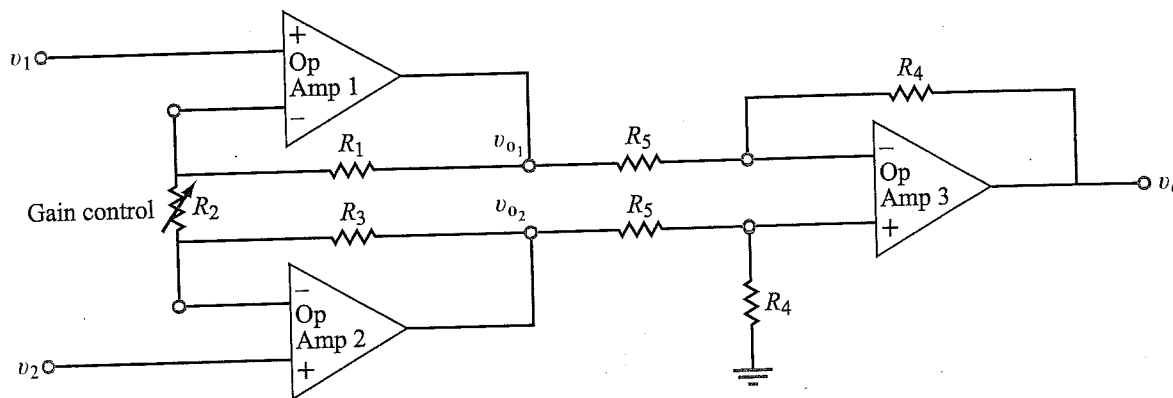


Figure 4-20: Instrumentation-amplifier circuit.

where  $G_1$  is the circuit gain of the first stage (which includes op amps 1 and 2) and is given by

$$G_1 = \frac{R_1 + R_2 + R_3}{R_2}. \quad (4.53)$$

The third op amp is a difference amplifier that amplifies  $(v_{o2} - v_{o1})$  by a gain factor  $G_2$  given by

$$G_2 = \frac{R_4}{R_5}. \quad (4.54)$$

Hence,

$$\begin{aligned} v_o &= G_2 G_1 (v_2 - v_1) \\ &= \left( \frac{R_4}{R_5} \right) \left( \frac{R_1 + R_2 + R_3}{R_2} \right) (v_2 - v_1). \end{aligned} \quad (4.55)$$

To simplify the circuit—and improve precision—all resistors—with the exception of  $R_2$ —often are chosen to be identical in design and construction, thereby minimizing deviations between their resistances. If we set  $R_1 = R_3 = R_4 = R_5 = R$  in Eq. (4.55), the expression for  $v_o$  reduces to

$$v_o = \left( 1 + \frac{2R}{R_2} \right) (v_2 - v_1). \quad (4.56)$$

In that case,  $R_2$  becomes the *gain-control resistance* of the circuit; its value (relative to  $R$ ) sets the gain. If the expected signal deviation  $(v_2 - v_1)$  is on the order of microvolts to


millivolts, the instrumentation amplifier is designed to have an overall gain that would amplify the signal to the order of volts.

► The instrumentation amplifier is a high-sensitivity, high-gain, deviation sensor. Several semiconductor manufacturers offer instrumentation-amplifier circuits in the form of integrated packages. ◀

**Concept Question 4-15:** When designing a multistage op-amp circuit, what should the design engineer do to insure that none of the op amps is driven into saturation?

**Concept Question 4-16:** If the goal is to measure small deviations between a pair of input signals, what is the advantage of using an instrumentation amplifier over using a difference amplifier?

**Exercise 4-8:** To monitor brain activity, an instrumentation-amplifier sensor uses a pair of needle-like probes inserted at different locations in the brain to measure the voltage difference between them. If the circuit is of the type shown in Fig. 4-20 with  $R_1 = R_3 = R_4 = R_5 = R = 50 \text{ k}\Omega$ ,  $V_{cc} = 12 \text{ V}$ , and the maximum magnitude of the voltage difference that the brain is likely to exhibit is 3 mV, what should  $R_2$  be to maximize the sensitivity of the brain sensor?

**Answer:**  $R_2 = 25 \text{ }\Omega$ . (See )