



Problem Set 4

Due Date: Sat Oct 17 2015
by 9 PM

Name: Solutions

Lab Section & TF: _____

Collaborators: _____

For Grading Purposes Only:

Q1: _____ / 10


Q2: _____ / 10

Q3: _____ / 15

Q4: _____ / 10

Q5: _____ / 5


Total: _____ / 50

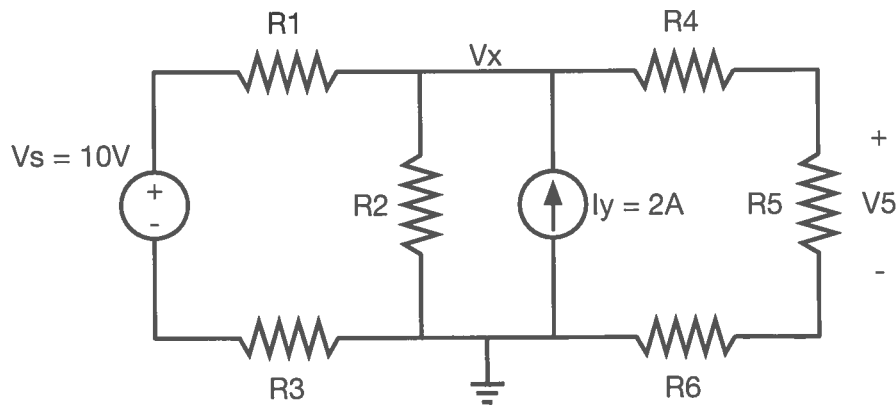Problem 1: Circuit Analysis (10 points)

Assume the following resistances: $R_1=R_3=1\Omega$, $R_2=2\Omega$, $R_4=R_6=2\Omega$, and $R_5=1\Omega$.

- a. (5 points) For the circuit above, solve for V_x and V_5 using the **node voltage method**.

First, redraw to simplify.

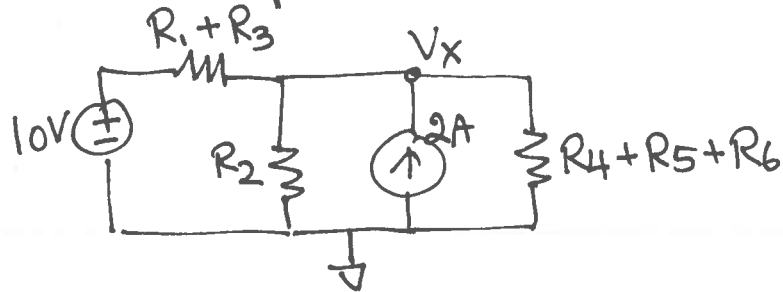

KCL @ V_x gives

$$\frac{10 - V_x}{R_1 + R_3} - \frac{V_x}{R_2} + 2A - \frac{V_x}{R_4 + R_5 + R_6} = 0$$

$$V_x \left(\frac{1}{R_1 + R_3} + \frac{1}{R_2} + \frac{1}{R_4 + R_5 + R_6} \right) = \frac{10}{R_1 + R_3} + 2$$

$$V_x \left(\frac{1}{2} + \frac{1}{2} + \frac{1}{5} \right) = \frac{10}{2} + 2 = 7$$



$$V_x \cdot \frac{12}{10} = 7 \Rightarrow \boxed{V_x = \frac{35}{6} \text{ V}}$$

Voltage divider gives...

$$V_5 = \frac{R_5}{R_4 + R_5 + R_6} \cdot V_x = \frac{1}{5} \cdot \frac{35}{6} \Rightarrow \boxed{V_5 = \frac{7}{6} \text{ V}}$$

b. (5 points) Now, solve for V_x and V_5 using **superposition**.

First solve for V_s and assume $I_y = 0$

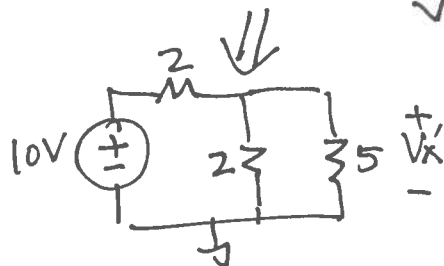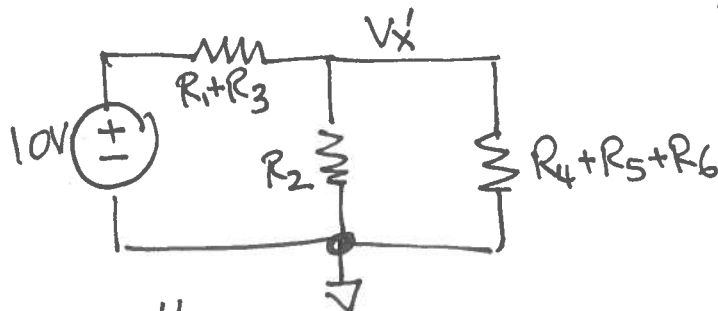

$$V_x' = \frac{2 || 5}{2 + 2 || 5} \cdot 10V$$

$$= \frac{10/7 \cdot 10}{2 + 10/7} = \frac{100}{24}$$

$$\boxed{V_x' = \frac{25}{6} V.}$$

Then solve for $I_y = 2$ + $V_s = 0$.



$$V_x'' = (2 || 2 || 5) \cdot 2A$$


$$= \frac{2}{\frac{1}{2} + \frac{1}{2} + \frac{1}{5}} = \frac{20}{12}$$

$$V_x = V_x' + V_x'' = \boxed{35/6}$$

$$\Leftarrow \boxed{V_x'' = 5/3}$$


$$\text{again, } V_5 = \frac{R_5}{R_4 + R_5 + R_6} V_x$$

$$= \boxed{7/6 V}$$

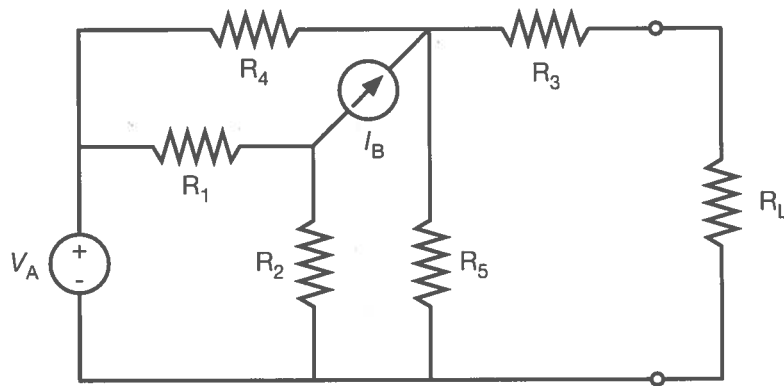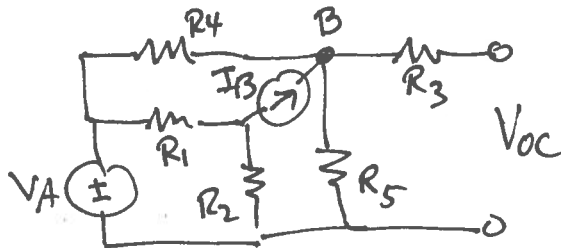Problem 2: Thevenin Equivalent Circuit (10 points)

(10 points) For the circuit shown above, find the Thevenin equivalent circuit from the perspective of R_L . Please find V_{THEV} and R_{THEV} in terms of V_A , I_B , and R_{1-5} .

To find V_{THEV} , solve for open-circuit voltage. (V_{oc})



$$V_{oc} = V_B$$

KCL @ node B ...


$$\frac{V_A - V_B}{R_4} + I_B = \frac{V_B}{R_5}$$

$$\frac{V_A}{R_4} + I_B = \left(\frac{1}{R_4} + \frac{1}{R_5}\right) V_B$$

$$V_{oc} = V_B = \left(\frac{V_A}{R_4} + I_B\right) \left(\frac{1}{R_4} + \frac{1}{R_5}\right)^{-1}$$

$$V_{THEV} = \left(\frac{V_A}{R_4} + I_B\right) \left(\frac{1}{R_4} + \frac{1}{R_5}\right)^{-1}$$

SHORT THE OUTPUT + FIND I_{SC}

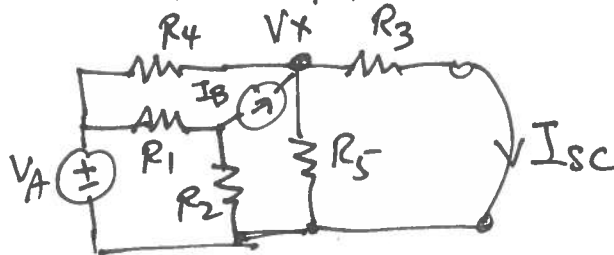

$$R_{THEV} = \frac{V_{THEV}}{I_{SC}}$$

$$R_{THEV} = \frac{V_{THEV}}{V_x / R_3}$$

KCL @ V_x gives


$$\frac{V_A - V_x}{R_4} + I_B = \frac{V_x}{R_5} + \frac{V_x}{R_3}$$

$$V_x = \left(\frac{V_A}{R_4} + I_B\right) \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}\right)^{-1}$$

$$I_{SC} = V_x / R_3$$


$$R_{THEV} = \frac{R_3 \left(\frac{1}{R_4} + \frac{1}{R_5}\right)^{-1}}{\left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5}\right)^{-1}}$$

Problem 3: RC Circuit (15 points)

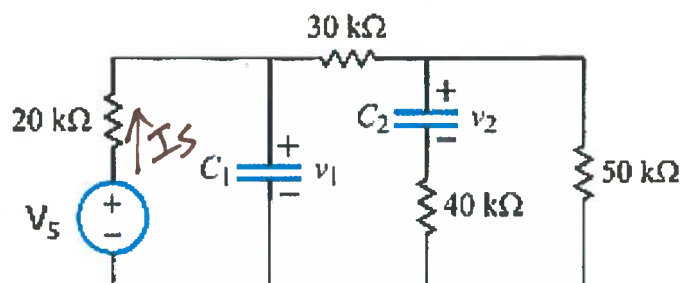

For the circuit shown above, find v_1 , v_2 , and the *current* through the voltage source for two conditions below.

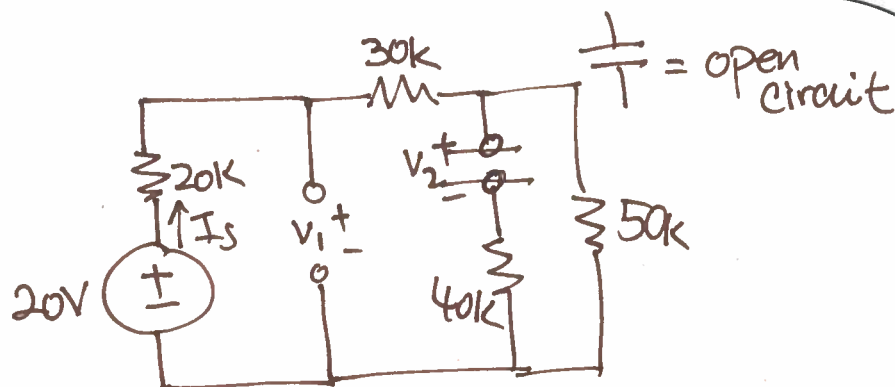- a. (5 points) The voltage source is a DC source (e.g., battery) with $V_s = 20V$.



$$V_1 = \frac{30K + 50K}{20K + 30K + 50K} \cdot 20 = \boxed{16V}$$

$$V_2 = \frac{50}{100} \cdot 20 = \boxed{10V}$$

$$I_s = \frac{V_s}{100K} = \frac{20}{100K} = \boxed{0.2mA}$$

- b. (5 points) The voltage source, V_s , is an AC source $V_s = 20\sin(2\pi ft)$, where f is very high frequency relative to the RC time constants of this circuit.

at high frequency, $C \rightarrow$ short circuit
therefore $V_1 = V_2 = \phi V$

$$I_{sc} = \frac{V_s}{20K} = \frac{20}{20K} \cdot \sin(2\pi ft)$$

- c. (5 points) Calculate the average power delivered by the source for both (a) and (b) above.

$$(a) P = I \cdot V = \frac{1}{5} \cdot 20 = \boxed{4W}$$

$$(b) P = \frac{V_{RMS}^2}{R} \quad \text{where } V_{RMS} = \frac{V_{amplitude}}{\sqrt{2}}$$


From
Lecture 3

$$P = \frac{20^2}{2(20K)} = \frac{400}{40K} = \frac{1}{100}$$

$\boxed{\text{or } 10mW}$

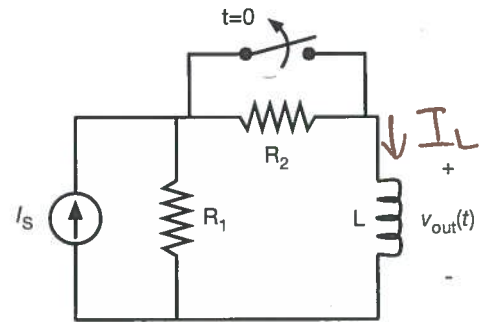Problem 4: Step Response of RL Circuit (10 points)

Please refer to the circuit shown (to the right) and answer the questions the below. The switch has been closed for a long time and opens at $t = 0$ and remains open. Please provide your answers in terms of I_s , R_1 , R_2 and L .



- a. (2 points) What is the current flowing through the inductor, L , at $t=0^-$ and $t=\infty$?

at $t=0^-$
 $I_L = I_s$


at $t=\infty$
 $I_L = \frac{R_1}{R_1 + R_2} I_s$
 Current divider

- b. (3 points) What is the current flowing through R_1 and R_2 at $t=0^-$ and $t=\infty$?

at $t=0^-$
 $I_{R_1} = 0$
 $I_{R_2} = 0$

at $t=\infty$
 $I_{R_1} = \frac{R_2}{R_1 + R_2} I_s$
 $I_{R_2} = \frac{R_1}{R_1 + R_2} I_s$

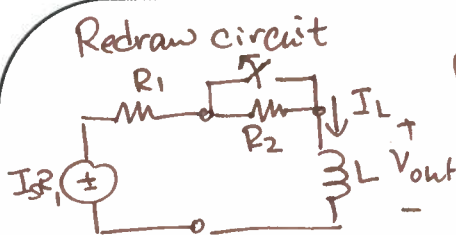- c. (5 points) Please sketch the voltage, $v_{out}(t)$, across the inductor vs. time.



At $t=0^-$, $V_{out} = 0$


But $I_L = I_s$

Also, at $t=\infty$


$V_{out} = 0$

$I_L = \frac{I_s R_1}{R_1 + R_2}$

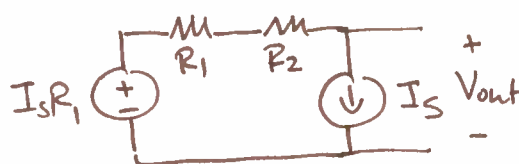at $t=0$ circuit looks like the following




$$\frac{I_s R_1 - V_{out}}{R_1 + R_2} = I_s \Rightarrow V_{out}(t=0) = -I_s R_2$$

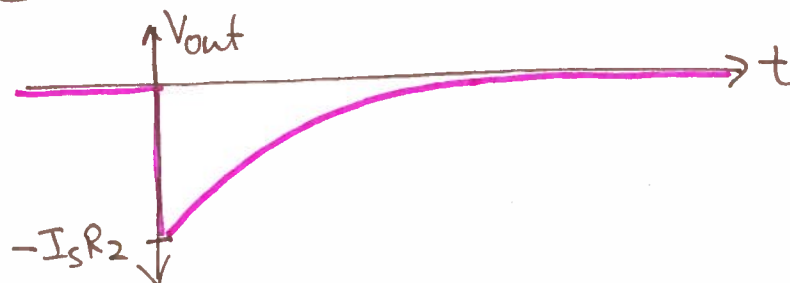

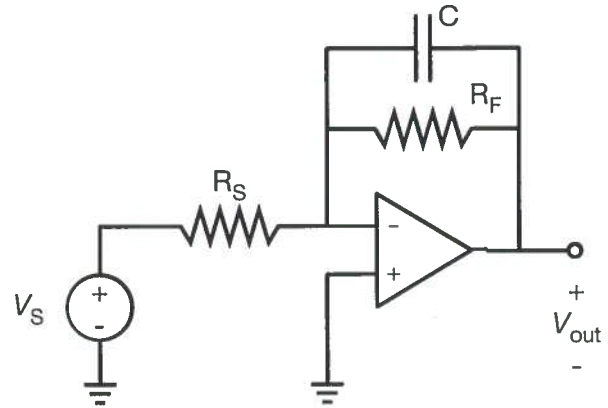Problem 5: Op-amp Circuit with C (5 points)

For this problem, assume V_s provides a unit voltage step, $u(t)$, 0V for $t < 0$ and transitions to 1V at $t = 0$ and stays at 1V for $t > 0$.



- a. (5 points) For the op-amp circuit, sketch the resulting waveform for V_{out} versus time.

$$\text{at } t = 0^-, V_s = 0 \rightarrow V_{out} = 0$$

$$\begin{aligned} \text{at } t = \infty, V_s = 1 \rightarrow V_{out} &= -\frac{R_F}{R_s} V_s \\ &= -\frac{R_F}{R_s} \end{aligned}$$

